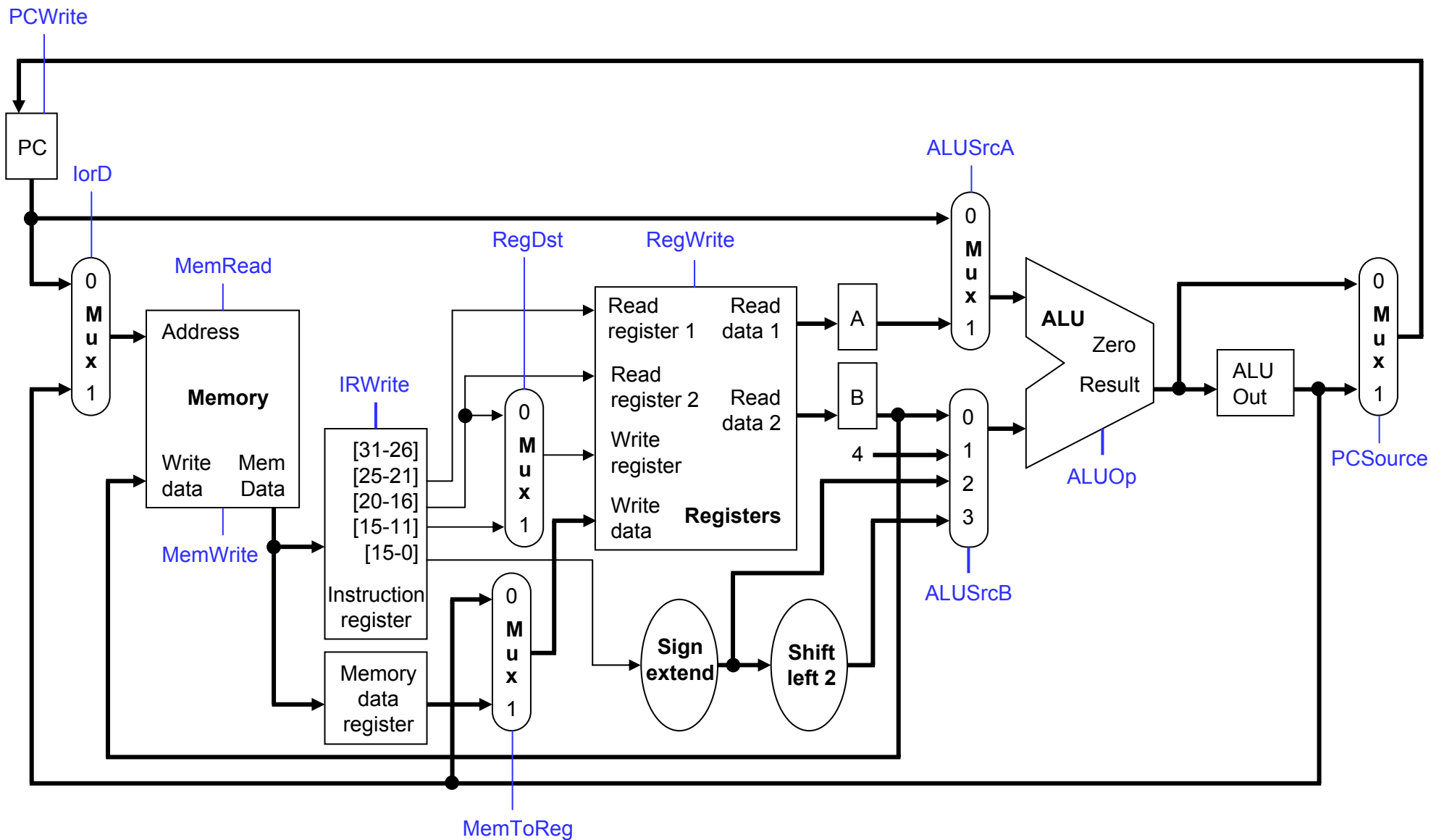


Multicycle control

- Last time we introduced a multicycle datapath, which addresses some of the performance and cost problems of a single-cycle datapath.
 - Instruction execution is divided into several steps.
 - Each instruction uses only as many steps as necessary.
 - Each step takes one clock cycle.
 - The datapath needs just one ALU and one memory.
- Today we'll show how to make this multicycle datapath go.
 - We present the correct control signals for each instruction.
 - Then we can design the control unit for generating those signals.



The multicycle datapath



Differences from the single-cycle datapath

- Two extra adders, and one of the memories, were removed.
- Some additional multiplexers are needed to control everything.
 - The ALU now operates on registers, memory displacements, branch offsets, and the PC.
 - A single memory contains both instructions and data, and the address is supplied by either the PC or the ALU.
- Since instructions need multiple cycles for execution, the PC is no longer updated on every clock cycle.
- Intermediate registers preserve data that's used in different cycles while executing one instruction. Since MDR, A, B and ALUOut only need to save data for one cycle, they are automatically written to on each cycle.

Executing a beq instruction

- We can execute a branch instruction in three stages or clock cycles.

beq \$t0, \$t1, offset

- **Stage 1** includes two actions which use two separate functional units: the memory and the ALU.
 - Fetch the instruction from memory and store it in IR.


$IR = Mem[PC]$

- Use the ALU to increment the PC by 4.

$PC = PC + 4$

- Again, the writes to IR and PC will occur on the next positive edge of the clock signal, at the *end* of the stage.

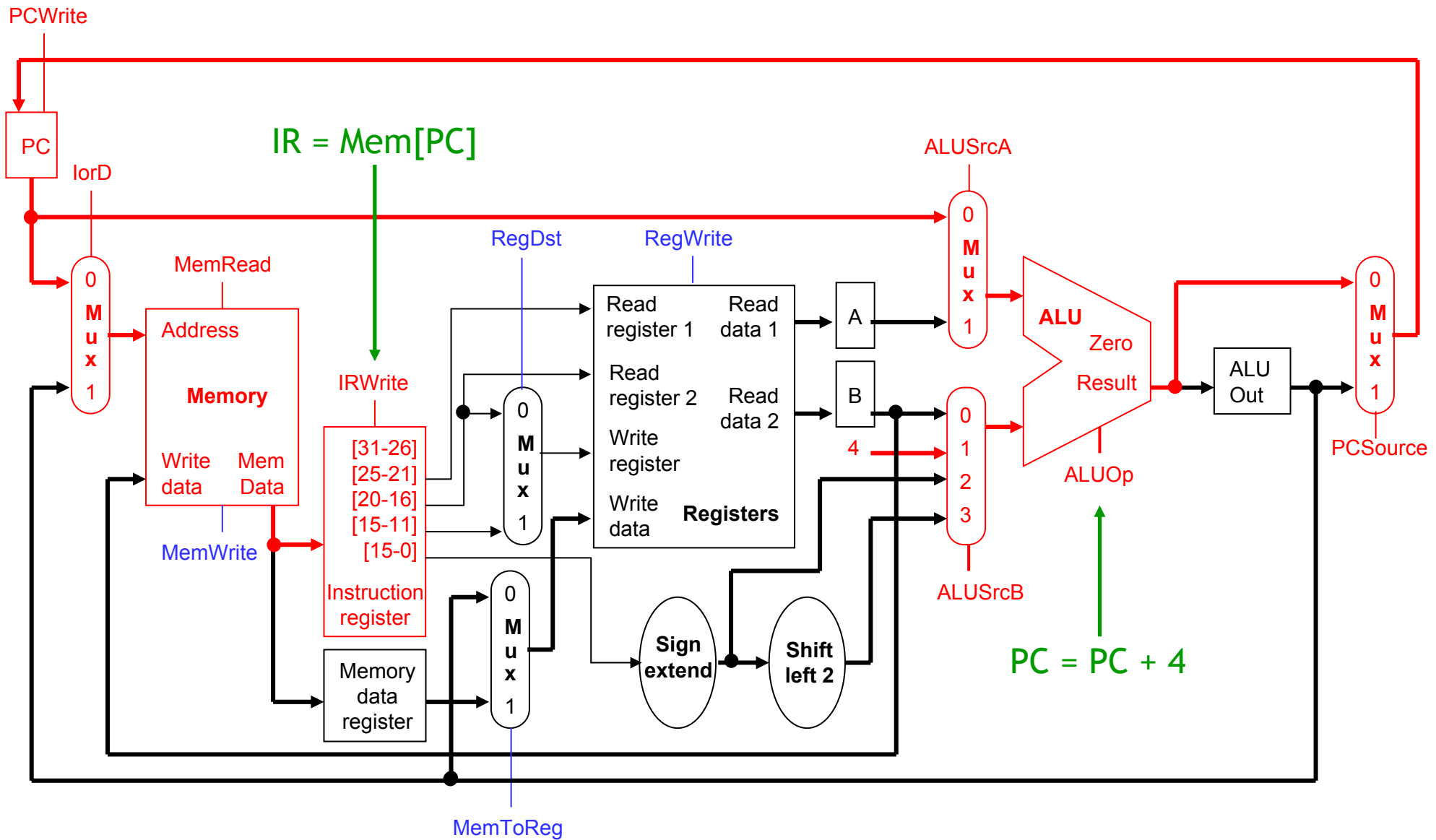Stage 1: Instruction fetch and PC increment



Stage 1 control signals

- Instruction fetch: $IR = Mem[PC]$

Signal	Value	Description
MemRead	1	Read from memory
lorD	0	Use PC as the memory read address
IRWrite	1	Save memory contents to instruction register

- Increment the PC: $PC = PC + 4$

Signal	Value	Description
ALUSrcA	0	Use PC as the first ALU operand
ALUSrcB	01	Use constant 4 as the second ALU operand
ALUOp	010	Perform addition
PCWrite	1	Change PC
PCSource	0	Update PC from the ALU output

- We'll assume that all control signals not listed are implicitly set to 0.

Read registers and compute the branch target

- **Stage 2** of the **beq** execution also includes two actions. Both actions can be done in the same cycle, since they use different functional units.
 - Read the contents of source registers *rs* and *rt*, and store them in the intermediate registers *A* and *B*. (Remember the *rs* and *rt* fields come from the instruction register *IR*.)

$$A = \text{Reg}[\text{IR}[25-21]]$$


$$B = \text{Reg}[\text{IR}[20-16]]$$

- Compute the branch target address by adding the new PC (the original PC + 4) to the sign-extended, shifted constant from *IR*.

$$\text{ALUOut} = \text{PC} + (\text{sign-extend}(\text{IR}[15-0]) \ll 2)$$

We save the target address in *ALUOut* for now, since we don't know yet if the branch should be taken.

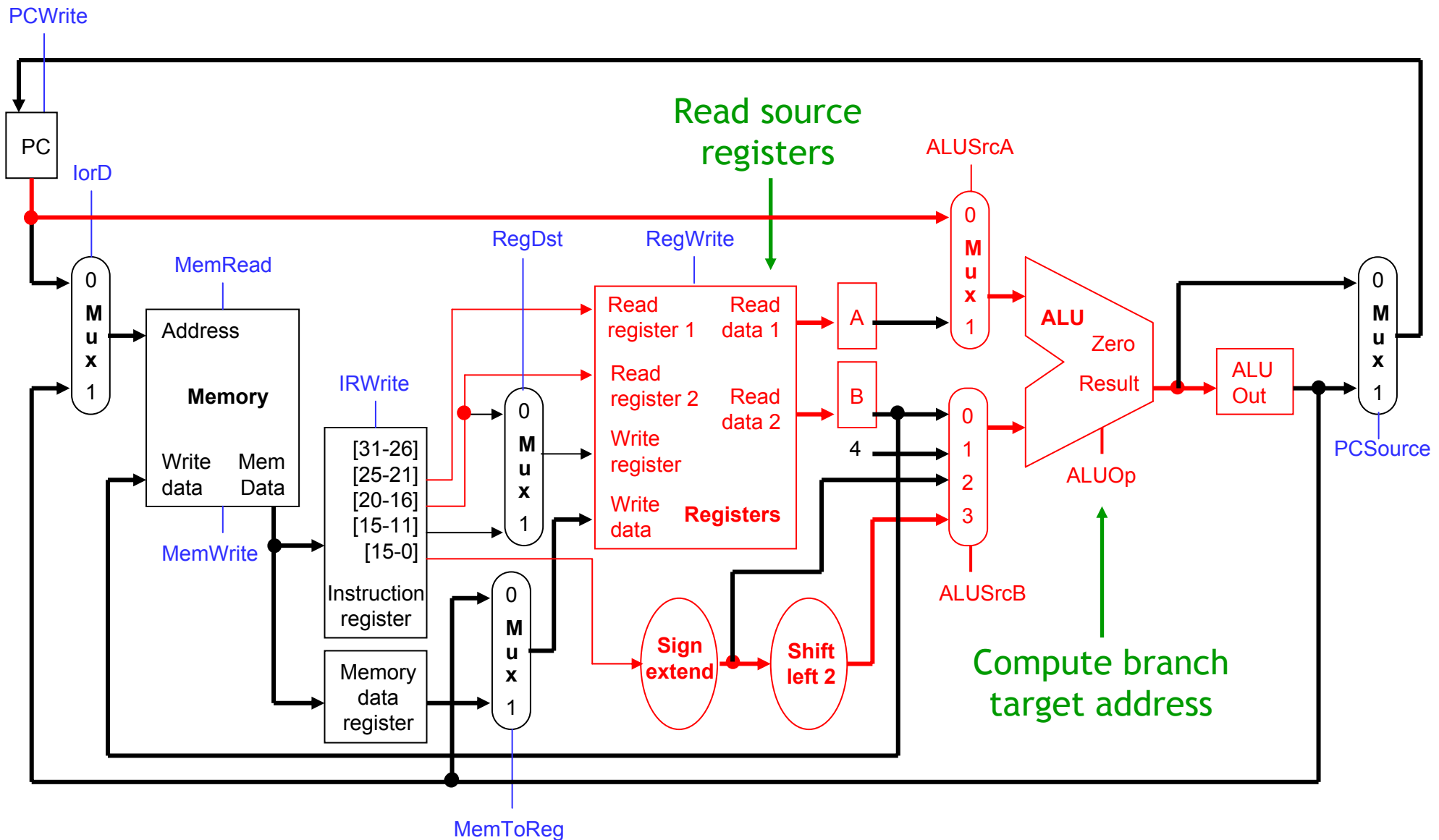Stage 2: Register fetch & branch target computation



Stage 2 control signals

- No other control signals need to be set for the register reading operations $A = \text{Reg}[\text{IR}[25-21]]$ and $B = \text{Reg}[\text{IR}[20-16]]$.
 - $\text{IR}[25-21]$ and $\text{IR}[20-16]$ are already applied to the register file.
 - Registers A and B are already written on every clock cycle.
- Branch target computation: $\text{ALUOut} = \text{PC} + (\text{sign-extend}(\text{IR}[15-0]) \ll 2)$

Signal	Value	Description
ALUSrcA	0	Use PC as the first ALU operand
ALUSrcB	11	Use $(\text{sign-extend}(\text{IR}[15-0]) \ll 2)$ as second operand
ALUOp	010	Add and save the result in ALUOut

ALUOut is also written automatically on each clock cycle.

Optimistic execution

- We don't know whether or not to take a branch until *after* we compare the values in intermediate registers A and B.
- But we can still go ahead and compute the branch target first. The book calls this **optimistic execution**.
 - The ALU is otherwise free during this clock cycle.
 - Nothing is harmed by doing the computation early. If the branch is not taken, we can just ignore the ALU result.
- This idea is also used in more advanced CPU design techniques.
 - Modern CPUs perform branch prediction, which we'll discuss in a few weeks in the context of pipelining.
 - The Intel IA-64 architecture and the Itanium processors go one step further with branch predication and data speculation.

Branch completion


- **Stage 3** is the final cycle needed for executing a branch instruction.

if (A == B) then
PC = ALUOut

- Remember that A and B are compared by subtracting and testing for a result of 0, so we must use the ALU again in this stage.



Stage 3 (beq): Branch completion

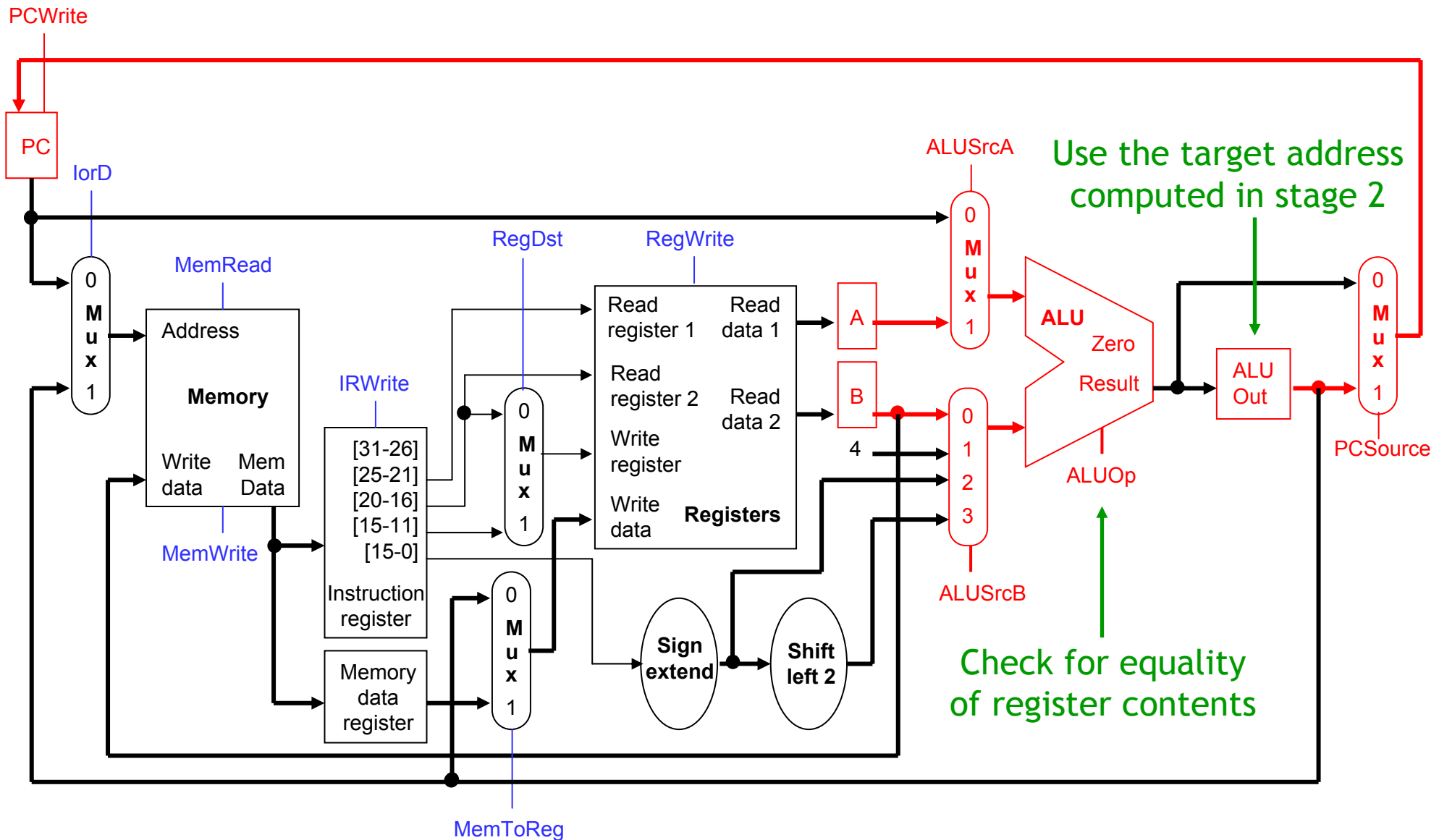

Stage 3 (beq) control signals

- Comparison: `if (A == B) ...`

Signal	Value	Description
ALUSrcA	1	Use A as the first ALU operand
ALUSrcB	00	Use B as the second ALU operand
ALUOp	110	Subtract, so Zero will be set if A = B

- Branch: `...then PC = ALUOut`

Signal	Value	Description
PCWrite	Zero	Change PC only if Zero is true (i.e., A = B)
PCSource	1	Update PC from the ALUOut register

- ALUOut contains the ALU result from the *previous* cycle, which would be the branch target. We can write that to the PC, even though the ALU is doing something different (comparing A and B) during the *current* cycle.

Executing arithmetic instructions

- What about an R-type instruction like `add $t1, $t1, $t2`?
- The first two stages are the same as for the branch.
 - **Stage 1** involves instruction fetch and PC increment.

$$IR = Mem[PC]$$

$$PC = PC + 4$$

- **Stage 2** is register fetch and branch target computation.

$$A = Reg[IR[25-21]]$$

$$B = Reg[IR[20-16]]$$

$$ALUOut = PC + (\text{sign-extend}(IR[15-0]) \ll 2)$$

- Hey Howard! R-type instructions don't branch!
 - But doing this optimistic computation in Stage 2 won't hurt anything.
 - It makes the handling of `beq` and R-type instructions more uniform.

Stages 3-4 (R-type): ALU execution and writeback

- **Stage 3** for an arithmetic instruction is simply ALU computation.

$$\text{ALUOut} = A \text{ op } B$$


- A and B are the intermediate registers holding the source operands.
- The ALU operation is determined by the instruction's "func" field and could be one of add, sub, and, or, slt.

- **Stage 4**, the final R-type stage, is to store the ALU result generated in the *previous* cycle into the destination register rd.


$$\text{Reg}[\text{IR}[15-11]] = \text{ALUOut}$$



Stage 3 (R-type): instruction execution

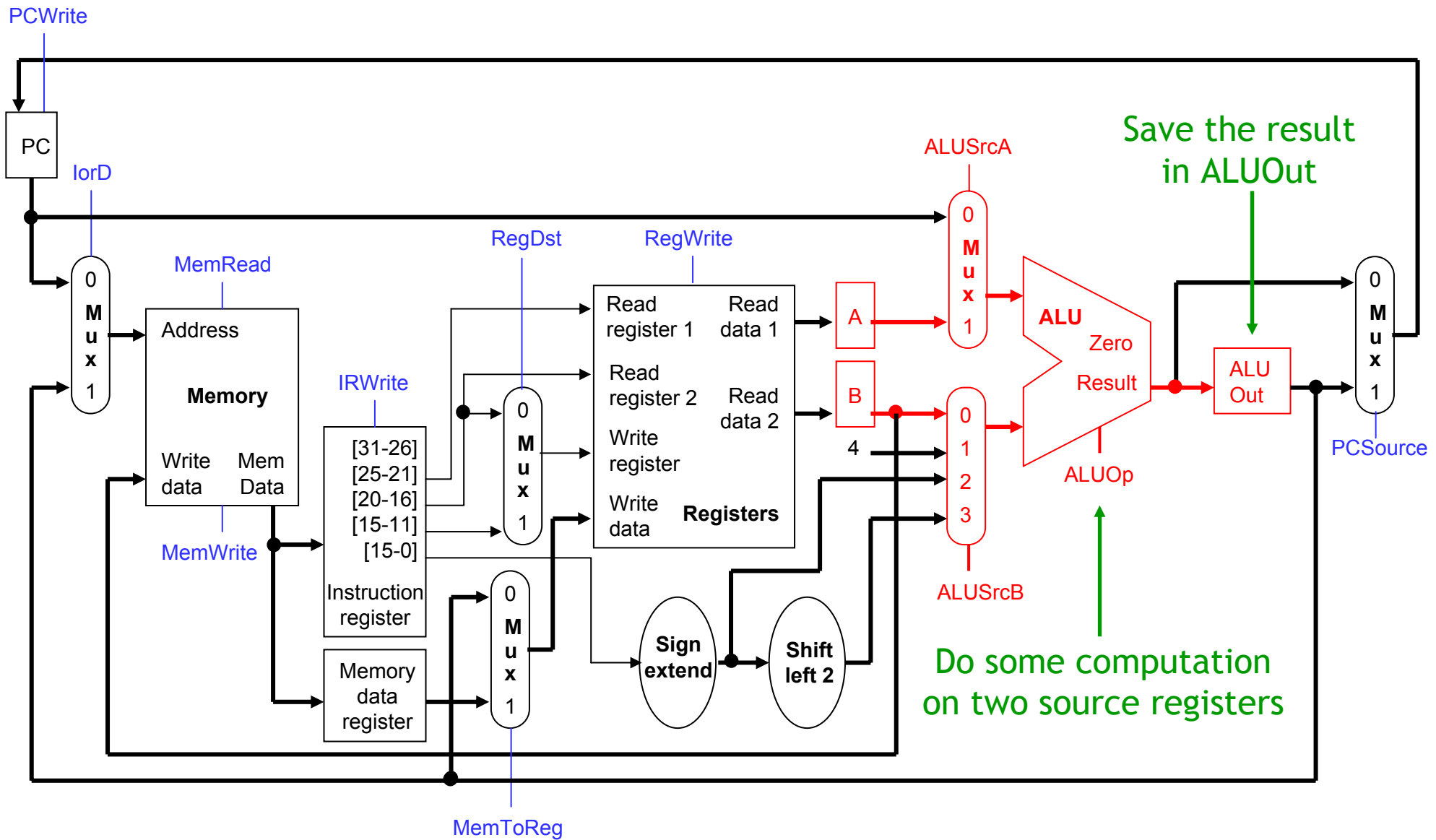

Stage 4 (R-type): write back

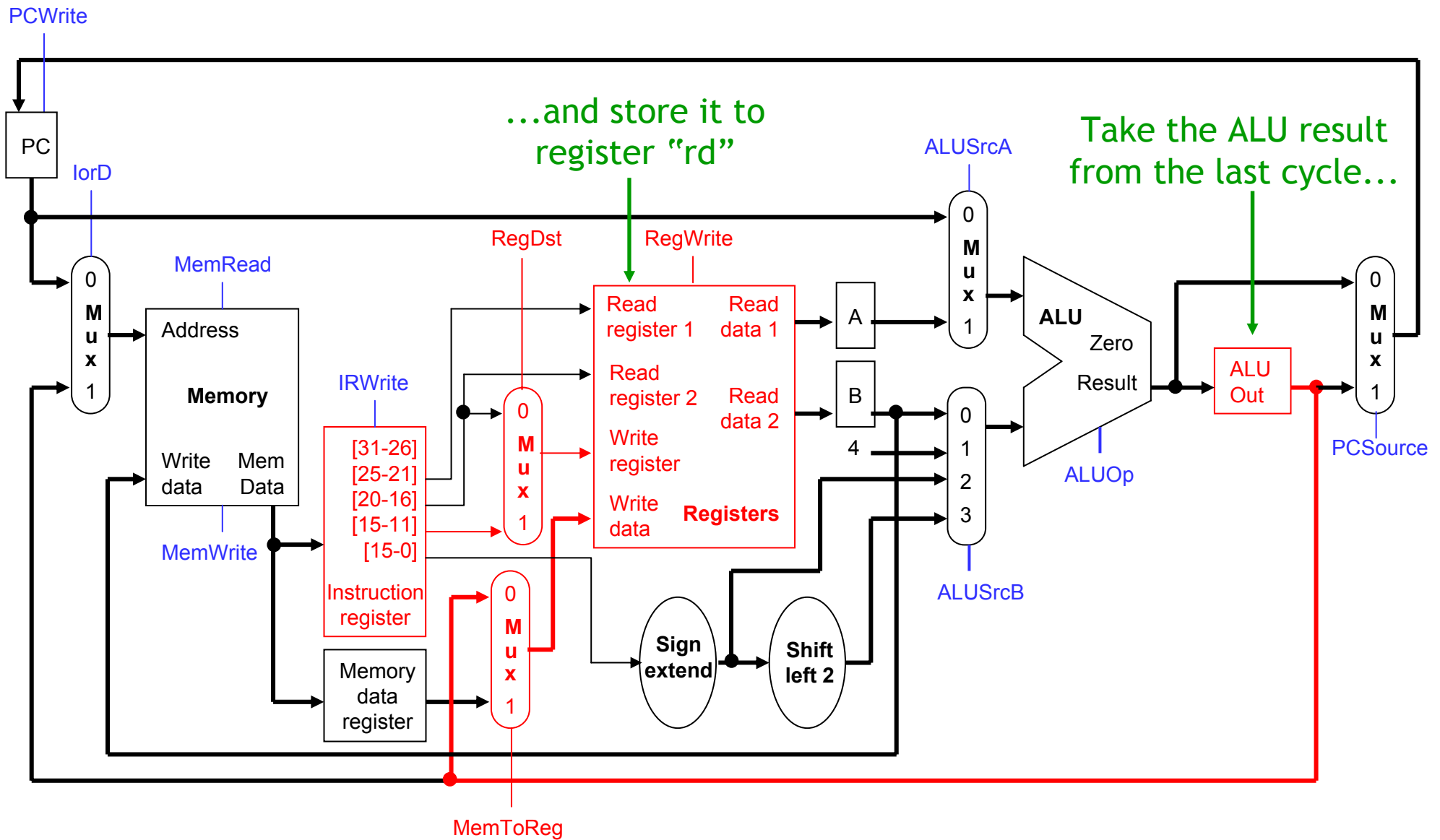

Stages 3-4 (R-type) control signals

- **Stage 3** (execution): $ALUOut = A \text{ op } B$

Signal	Value	Description
ALUSrcA	1	Use A as the first ALU operand
ALUSrcB	00	Use B as the second ALU operand
ALUOp	func	Do the operation specified in the "func" field

- **Stage 4** (writeback): $Reg[IR[15-11]] = ALUOut$

Signal	Value	Description
RegWrite	1	Write to the register file
RegDst	1	Use field rd as the destination register
MemToReg	0	ALUOut contains the data to write

Executing a sw instruction

- A store instruction, like `sw $a0, 16($sp)`, also shares the same first two stages as the other instructions.
 - **Stage 1**: instruction fetch and PC increment.
 - **Stage 2**: register fetch and branch target computation.
- **Stage 3** computes the effective memory address using the ALU.

$$\text{ALUOut} = A + \text{sign-extend}(\text{IR}[15-0])$$


A contains the base register (like `$sp`), and `IR[15-0]` is the 16-bit constant offset from the instruction word, which is *not* shifted.

- **Stage 4** saves the register contents (here, `$a0`) into memory.


$$\text{Mem}[\text{ALUOut}] = B$$

Again, remember that the second source register `rt` was already read in Stage 2, and its contents are in intermediate register B.

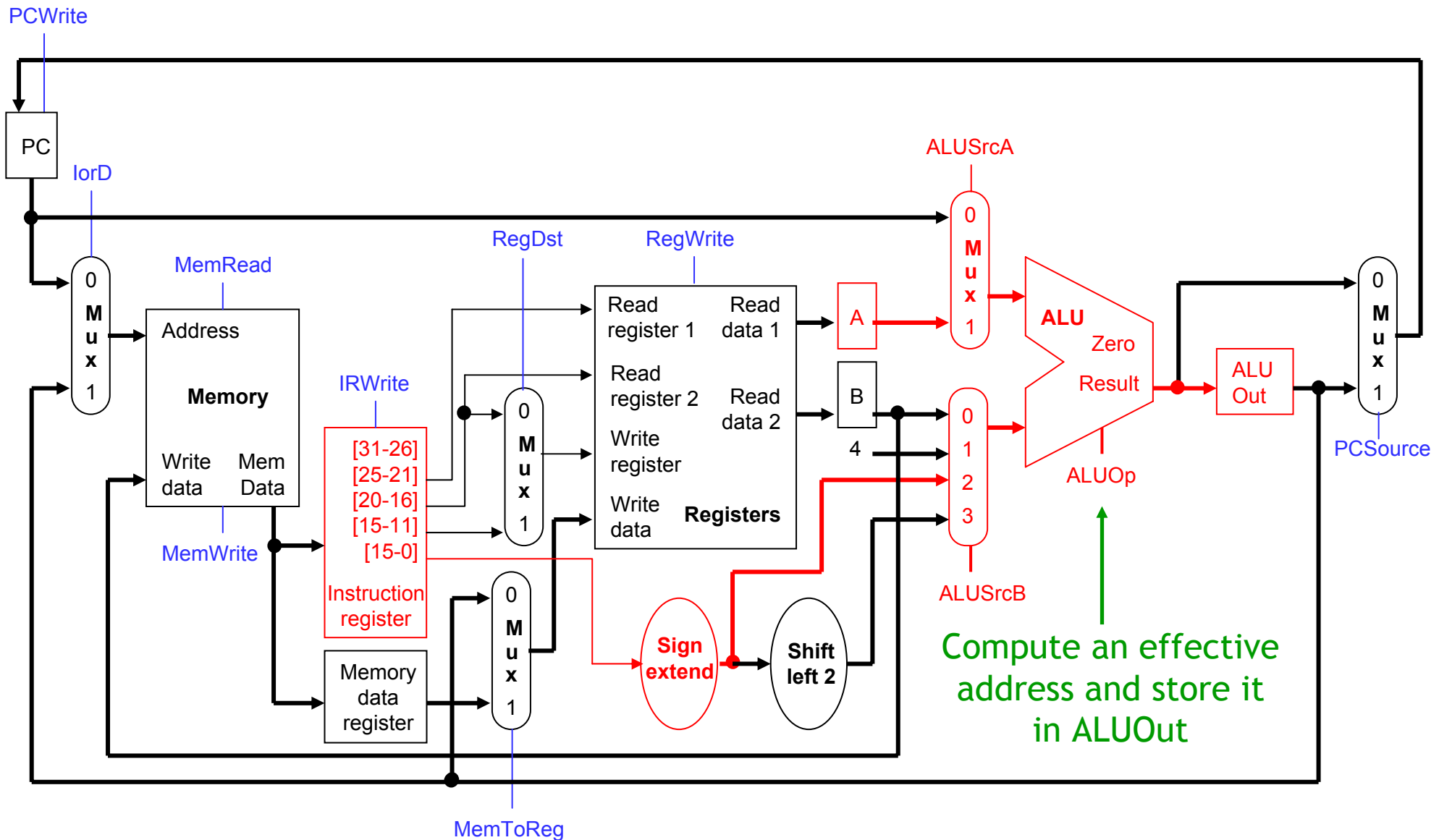Stage 3 (sw): effective address computation



Stage 4 (sw): memory write

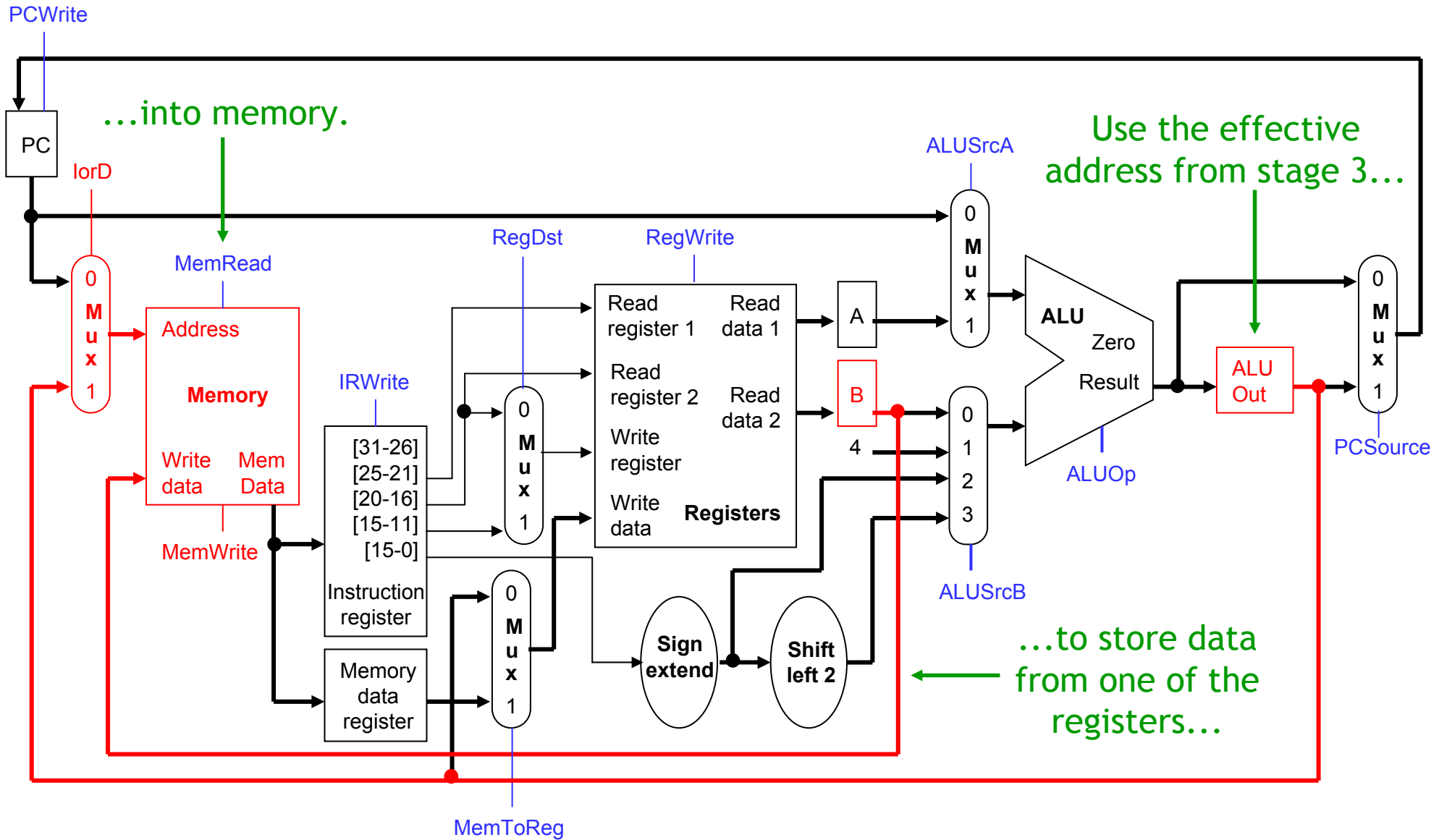

Stages 3-4 (sw) control signals

- **Stage 3** (address computation): $ALUOut = A + \text{sign-extend}(IR[15-0])$

Signal	Value	Description
ALUSrcA	1	Use A as the first ALU operand
ALUSrcB	10	Use sign-extend(IR[15-0]) as the second operand
ALUOp	010	Add and store the resulting address in ALUOut

- **Stage 4** (memory write): $Mem[ALUOut] = B$

Signal	Value	Description
MemWrite	0	Write to the memory
lorD	0	Use ALUOut as the memory address

The memory's "Write data" input *always* comes from the B intermediate register, so no selection is needed.

Executing a lw instruction

- Finally, **lw** is the most complex instruction, requiring five stages.
- The first two are like all the other instructions.
 - **Stage 1**: instruction fetch and PC increment.
 - **Stage 2**: register fetch and branch target computation.
- The third stage is the same as for **sw**, since we have to compute an effective memory address in both cases.
 - **Stage 3**: compute the effective memory address.



Stages 4-5 (lw): memory read and register write

- **Stage 4** is to read from the effective memory address, and to store the value in the intermediate register MDR (memory data register).


$$\text{MDR} = \text{Mem}[\text{ALUOut}]$$

- **Stage 5** stores the contents of MDR into the destination register.


$$\text{Reg}[\text{IR}[20-16]] = \text{MDR}$$

Remember that the destination register for lw is field *rt* (bits 20-16) and *not* field *rd* (bits 15-11).

Stage 4 (lw): memory read

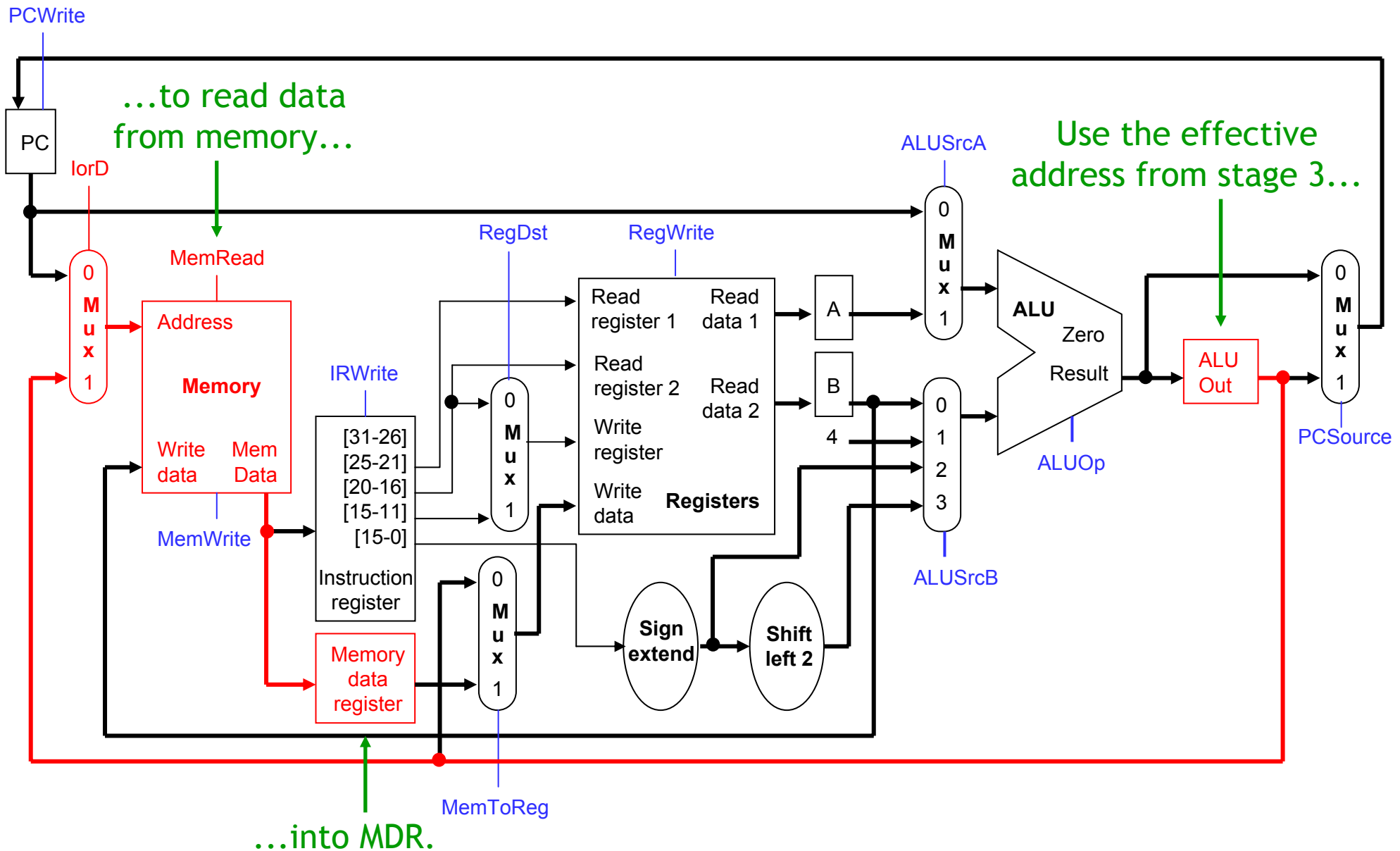

Stage 5 (lw): register write

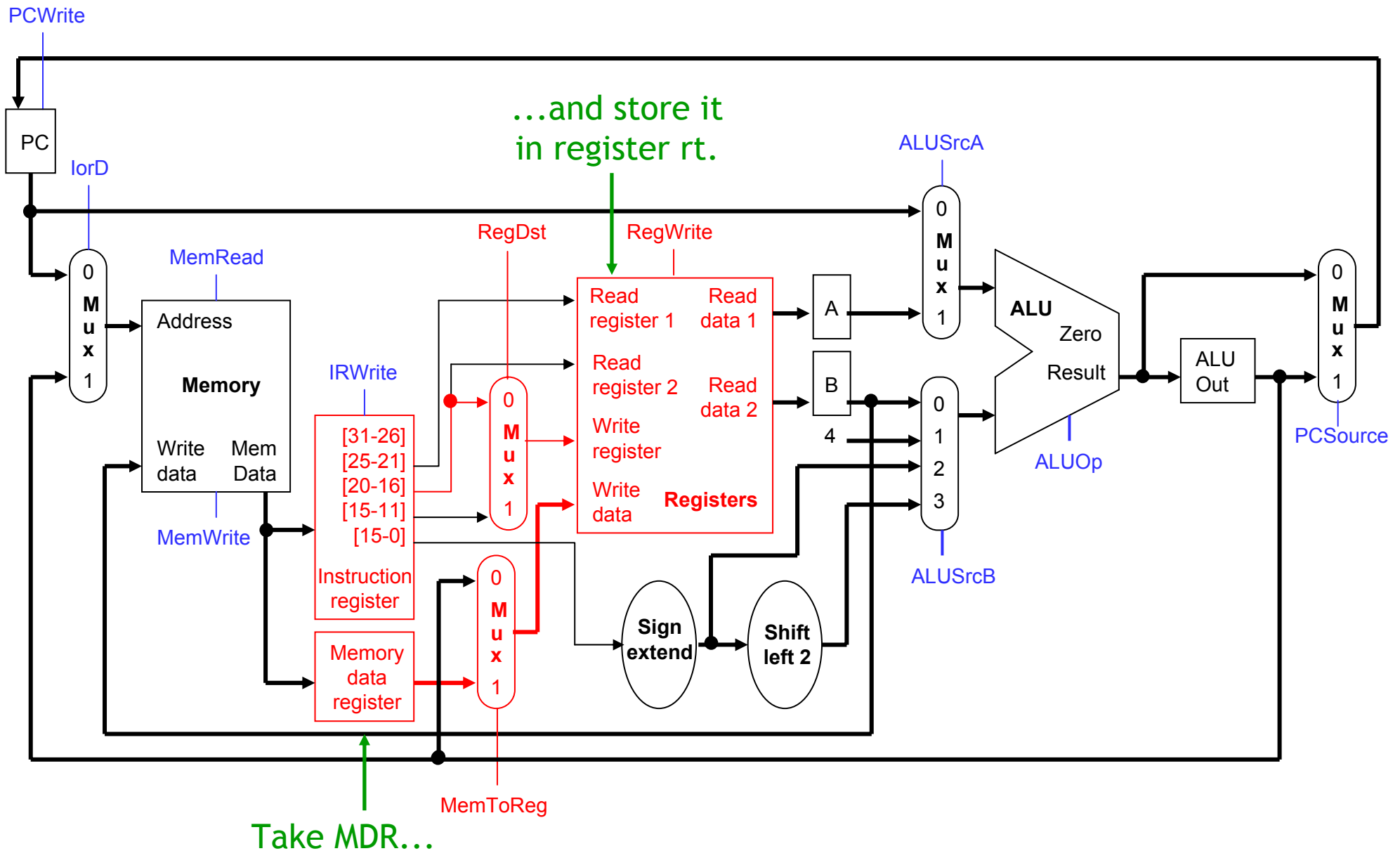

Stages 4-5 (lw) control signals

- **Stage 4** (memory read): $MDR = Mem[ALUOut]$

Signal	Value	Description
MemRead	1	Read from memory
lrd	1	Use ALUOut as the memory address

The memory contents will be automatically written to MDR.


- **Stage 5** (writeback): $Reg[IR[20-16]] = MDR$

Signal	Value	Description
RegWrite	1	Store new data in the register file
RegDst	0	Use field rt as the destination register
MemToReg	1	Write data from MDR (from memory)

Multicycle control unit

- The control unit is responsible for producing all of these control signals.
- Each instruction requires a *sequence* of control signals, generated over multiple clock cycles.
 - This implies that we need a **state machine**.
 - The datapath control signals will be **outputs** of the state machine.
- Different instructions require different sequences of steps.
 - This implies the instruction word is an **input** to the state machine.
 - The **next state** depends upon the exact instruction being executed.
- After we finish executing one instruction, we'll have to repeat the entire process again to execute the next instruction.

 Finite-state machine for the control unit



Implementing the FSM

- This can be translated into a state table; here are the first two states.

Current State	Input (Op)	Next State	Output (Control signals)											
			PC Write	lorD	Mem Read	Mem Write	IR Write	Reg Dst	MemTo Reg	Reg Write	ALU SrcA	ALU SrcB	ALU Op	PC Source
Instr Fetch	X	Reg Fetch	1	0	1	0	1	X	X	0	0	01	010	0
Reg Fetch	BEQ	Branch compl	0	X	0	0	0	X	X	0	0	11	010	X
Reg Fetch	R-type	R-type execute	0	X	0	0	0	X	X	0	0	11	010	X
Reg Fetch	LW/S W	Compute eff addr	0	X	0	0	0	X	X	0	0	11	010	X

- You can implement this the hard way.
 - Represent the current state using flip-flops or a register.
 - Find equations for the next state and (control signal) outputs in terms of the current state and input (instruction word).
- Or you can use the easy way.
 - Stick the whole state table into a memory, like a ROM or a PLA.
 - This would be much easier, since you don't have to derive equations.

Summary

- Generating control signals for the multicycle datapath is complicated!
 - Each instruction takes several cycles to execute.
 - Different instructions require different control signals and a different number of cycles.
 - We have to provide the control signals in the right sequence.
- Next time we'll finish talking about the multicycle processor.
 - **Microprogramming** is another way to implement control units.
 - We'll also examine the performance of this multicycle approach.

