

# Addition and multiplication


---

- Arithmetic is the most basic thing you can do with a computer, but it's not as easy as you might expect!
- These next few lectures focus on addition, subtraction, multiplication and arithmetic-logic units or ALUs, which are the “heart” of CPUs.
- Arithmetic hardware is an excellent example of many issues that we've discussed, such as Boolean algebra, circuit analysis, data representation, and hierarchical, modular design.


 
# Binary addition by hand

- You can add two binary numbers one column at a time starting from the right, just like you add two decimal numbers.
- But remember it's binary. For example,  $1 + 1 = 10$  and you have to carry!





# Adding two bits


- We'll make a hardware adder based on our human addition algorithm.
- We start with a **half adder**, which adds two bits X and Y and produces a two-bit result: a **sum** S (the right bit) and a **carry out** C (the left bit).
- Here are truth tables, equations, circuit and block symbol.

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$C = XY$$

$$S = X'Y + XY'$$
$$= X \oplus Y$$

  

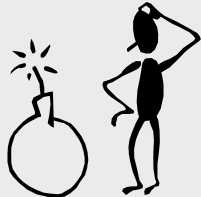

Be careful! Now we use + for both arithmetic addition and the logical OR operation.

# Adding three bits

- But what we really need to do is add *three* bits: the augend and addend bits, *and* the carry in from the right.
- A **full adder** circuit takes three inputs  $X$ ,  $Y$  and  $C_{in}$ , and produces a two-bit output consisting of a sum  $S$  and a carry out  $C_{out}$ .
- This truth table should look familiar, as it was an example in the decoder and multiplexer lectures.

$$\begin{array}{r} \phantom{+} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \\ \phantom{+} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \\ + \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \\ \hline \phantom{0} \phantom{0} \phantom{0} \phantom{0} \phantom{0} \end{array}$$

The diagram shows a vertical addition of three bits. The top row has four bits: 1, 1, 1, and 0. The second row has three bits: 1, 0, and 1. The third row has four bits: 1, 1, 1, and 0. A horizontal line is drawn below the third row. The bottom row has five bits: 1, 1, 0, 0, and 1. A blue oval highlights the 0 in the fourth column of the top row and the 0 in the fourth column of the bottom row.

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# Full adder equations

- Using Boolean algebra, we can simplify  $S$  and  $C_{out}$  as shown here.

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned} S &= \Sigma m(1,2,4,7) \\ &= X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in} \\ &= X'(Y'C_{in} + YC_{in}') + X(Y'C_{in}' + YC_{in}) \\ &= X'(Y \oplus C_{in}) + X(Y \oplus C_{in})' \\ &= X \oplus Y \oplus C_{in} \end{aligned}$$



$$\begin{aligned} C_{out} &= \Sigma m(3,5,6,7) \\ &= X'YC_{in} + XY'C_{in} + XYC_{in}' + XYC_{in} \\ &= (X'Y + XY')C_{in} + XY(C_{in}' + C_{in}) \\ &= (X \oplus Y)C_{in} + XY \end{aligned}$$

- Notice that XOR operations simplify things a bit, but we had to resort to using algebra since it's hard to find XOR-based expressions with K-maps.

  
# Full adder circuit

- We write the equations this way to highlight the hierarchical nature of adder circuits—you can build a full adder by combining two half adders!


$$S = X \oplus Y \oplus C_{in}$$
$$C_{out} = (X \oplus Y) C_{in} + XY$$



# A four-bit adder

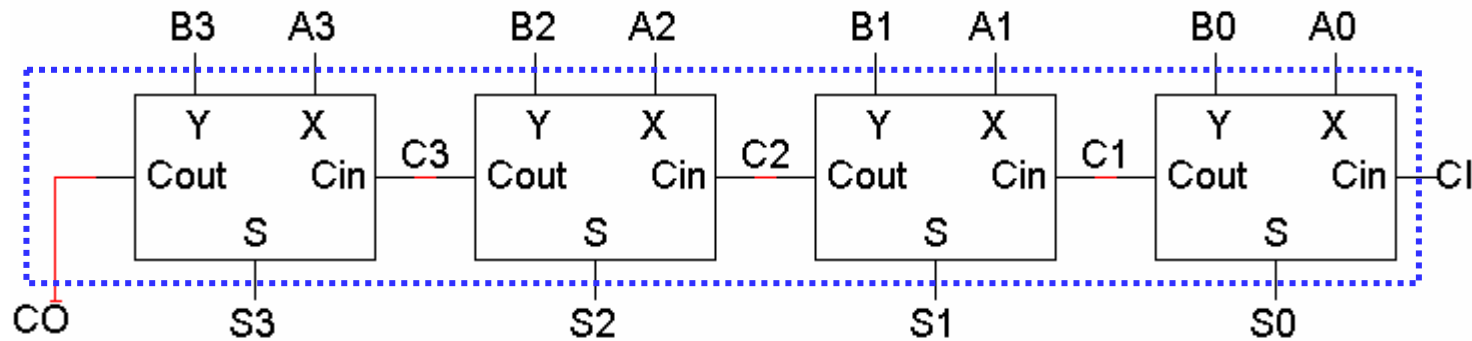


- Similarly, we can cascade four full adders to build a four-bit adder.
  - The inputs are two four-bit numbers ( $A_3A_2A_1A_0$  and  $B_3B_2B_1B_0$ ) and a carry in  $C_i$ .
  - The two outputs are a four-bit sum  $S_3S_2S_1S_0$  and the carry out  $C_o$ .
- If you designed this adder without taking advantage of the hierarchical structure, you'd end up with a 512-row truth table with five outputs!

 
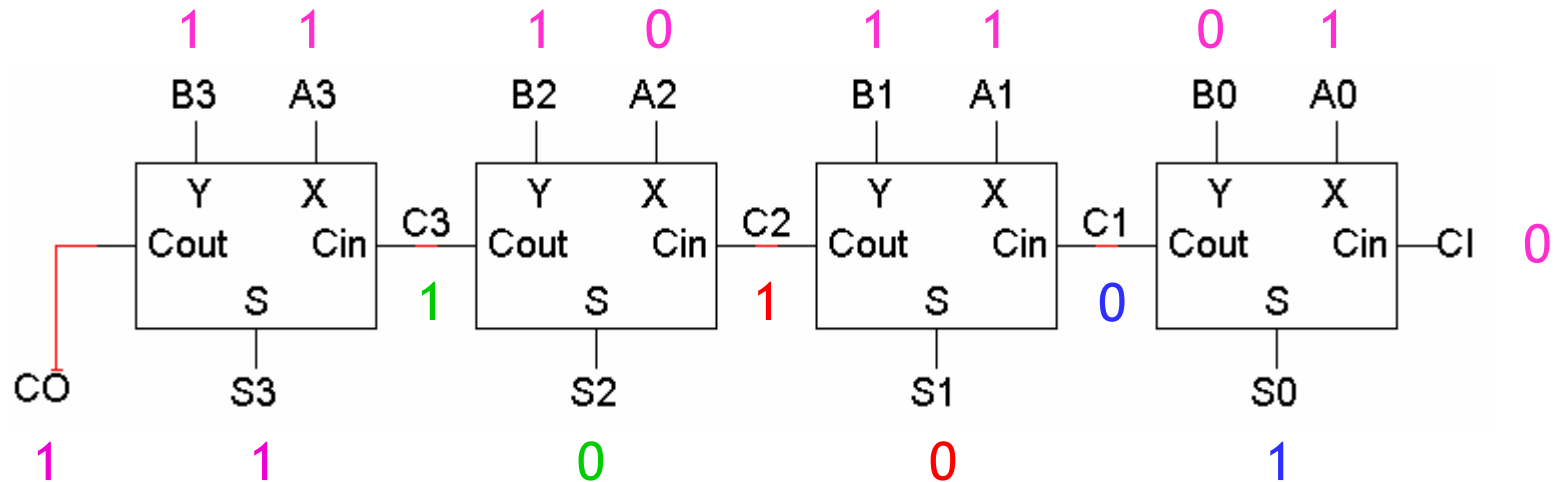
# An example of 4-bit addition

- Let's put our initial example into this circuit, with  $A=1011$  and  $B=1110$ .



1. Fill in all the inputs, including  $CI=0$
2. The circuit produces  $C1$  and  $S0$  ( $1 + 0 + 0 = 01$ )
3. Use  $C1$  to find  $C2$  and  $S1$  ( $1 + 1 + 0 = 10$ )
4. Use  $C2$  to compute  $C3$  and  $S2$  ( $0 + 1 + 1 = 10$ )
5. Use  $C3$  to compute  $CO$  and  $S3$  ( $1 + 1 + 1 = 11$ )


Woohoo! The final answer is 11001.


 
# Overflow

---

- This particular example illustrates a case of **overflow**.
  - The answer **11001** is *five* bits long, but the inputs **1011** and **1110** were each only four bits wide.
  - Although the five-bit answer 11001 is correct, we cannot use it in any subsequent computations with this four-bit adder.
- For “unsigned” addition, overflow occurs when the carry out is 1.
- Overflows can never be prevented because computer hardware is finite. Even though we can make adders of arbitrary sizes, there will always be another number that won't fit.



# Ariane 5


---

- In 1996, the European Space Agency's Ariane 5 rocket was launched for the first time... and it exploded 40 seconds after liftoff.
- It turns out the Ariane 5 used software designed for the older Ariane 4.
  - The Ariane 4 stored its horizontal velocity as a 16-bit signed integer.
  - But the Ariane 5 reaches a much higher velocity, which caused an overflow in the 16-bit quantity.
- The overflow error was never caught, so incorrect instructions were sent to the rocket boosters and main engine.


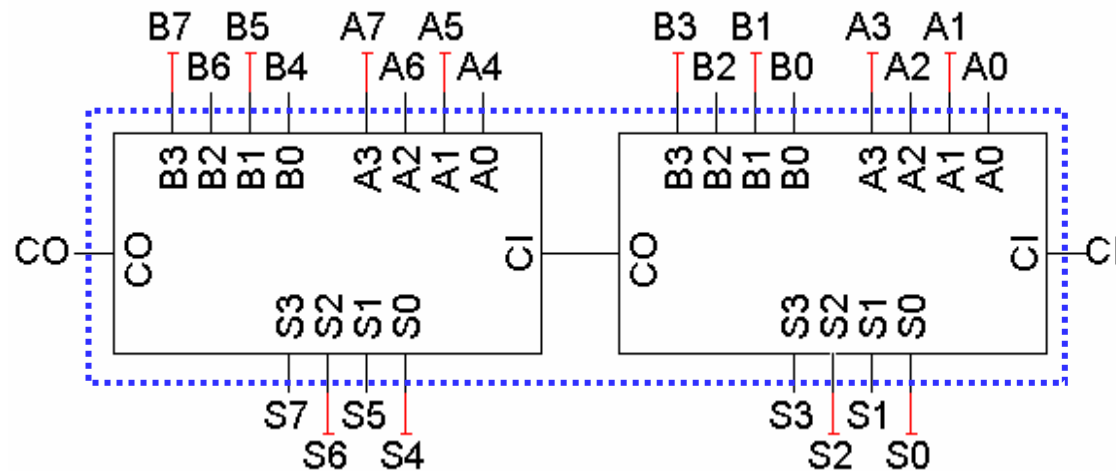
# Hierarchical adder design


- When you add two 4-bit numbers the carry in is always 0, so why does the four-bit adder have a CI input?
- We can use CI to combine four-bit adders together to make even larger adders, just like we combined half adders and full adders earlier.
- Here is one way to build an eight-bit adder, for example.



- CI is also useful for subtraction, as we'll see next time.
 
# Ripple carry delays

- The diagram below shows our four-bit adder completely drawn out.
- This is called a **ripple carry adder**, because the inputs A0, B0 and CI “ripple” leftwards until CO and S3 are produced.
- Ripple carry adders are slow!
  - There is a very long path from A0, B0 and CI to CO and S3.
  - For an  $n$ -bit ripple carry adder, the longest path has  $2n+1$  gates.
  - The longest path in a 64-bit adder would include 129 gates!



# A faster way to compute carry outs

- Instead of waiting for the carry out from each previous stage, we can minimize the delay by computing it directly with a two-level circuit.
- First we'll define two functions.
  - The “generate” function  $G_i$  produces 1 when there *must* be a carry out from position  $i$  (i.e., when  $A_i$  and  $B_i$  are both 1).


$$G_i = A_i B_i$$

- The “propagate” function  $P_i$  is true when an incoming carry is propagated (i.e, when  $A_i=1$  or  $B_i=1$ , but not both).

$$P_i = A_i \oplus B_i$$

- Then we can rewrite the carry out function.

$$C_{i+1} = G_i + P_i C_i$$

 

$A_i$	$B_i$	$C_i$	$C_{i+1}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

# Algebraic carry out hocus-pocus

- Let's look at the carry out equations for specific bits, using the general equation from the previous page  $C_{i+1} = G_i + P_i C_i$ .


$$C_1 = G_0 + P_0 C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 \\ &= G_1 + P_1(G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 \\ &= G_2 + P_2(G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$


$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3(G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

Ready to see the circuit?

 

- These expressions are all sums of products, so we can use them to make a circuit with only a two-level delay.

# A faster four-bit adder

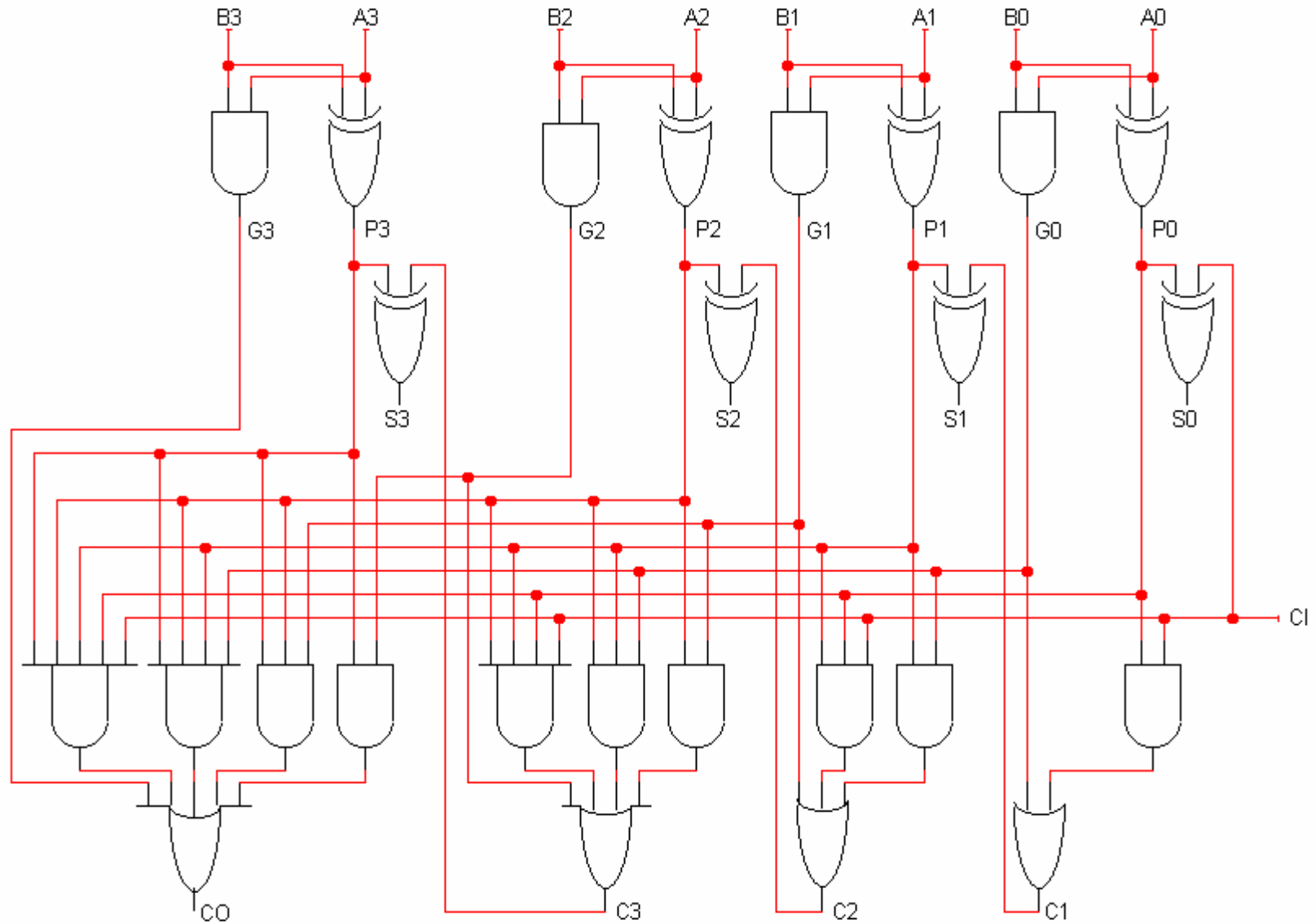

# Carry lookahead adders

---

- This is called a **carry lookahead adder**.
  - By adding more hardware, we reduced the number of levels in the circuit and sped things up.
  - We can combine carry lookahead adders just like ripple carry adders, and we can do carry lookahead *between* the adders too.
- How much faster is this?
  - For a four-bit adder, not much. There are 4 gates in the longest path of a carry lookahead adder, versus 9 gates for a ripple carry adder.
  - If we do the cascading properly, a 16-bit carry lookahead adder will have only 8 gates in the longest path, as opposed to 33 with a ripple carry adder.
  - The newest processors use 64-bit adders. That's 12 vs. 129 gates!
- The delay of a carry lookahead adder grows *logarithmically* with the size of the adder, while a ripple carry adder's delay grows *linearly*.





# Binary multiplication


				1	1	0	1	Multiplicand
				0	1	1	0	Multiplier
				0	0	0	0	}
			1	1	0	1	Partial products	
		1	1	0	1			
+	0	0	0	0				
	1	0	0	1	1	1	0	Product

- Since we always multiply by either 0 or 1, the **partial products** are always either **0000** or the multiplicand (**1101** in this example).
- There are four partial products which are added to form the result.
  - We can add them in pairs, using three adders.
  - The product can have up to 8 bits, but we can use four-bit adders if we stagger them leftwards, like the partial products themselves.


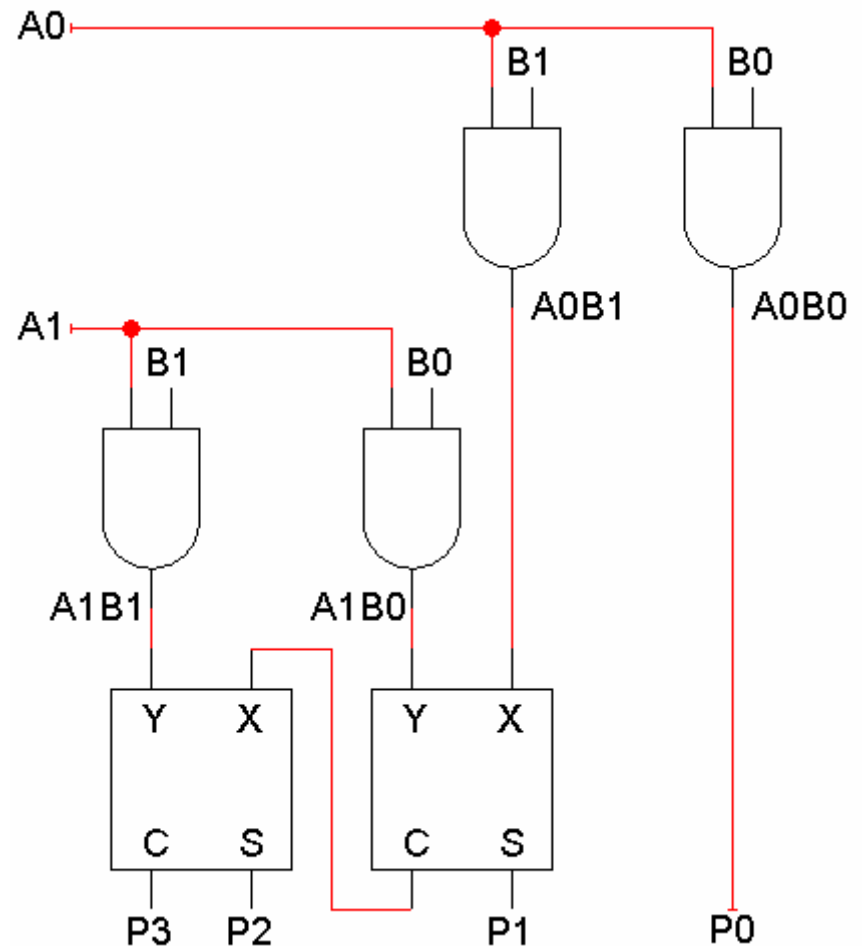
# A 2×2 binary multiplier


- Here is a circuit that multiplies the two-bit numbers  $A1A0$  and  $B1B0$ , resulting in the four-bit product  $P3-P0$ .
- For a 2×2 multiplier we can just use two half adders to sum the partial products. In general, though, we'll need full adders.
- The diagram on the next page shows how this can be extended to a four-bit multiplier, taking inputs  $A3-A0$  and  $B3-B0$  and outputting the product  $P7-P0$ .





# Complexity of multiplication circuits

---

 

- In general, when multiplying an  $m$ -bit number by an  $n$ -bit number:
  - There will be  $n$  partial products, one for each bit of the multiplier.
  - This requires  $n-1$  adders, each of which can add  $m$  bits.
- The circuit for 32-bit or 64-bit multiplication would be huge!

# Shifty arithmetic operations

---

- In decimal, an easy way to multiply by 10 is to shift all the digits to the left, and tack a 0 to the right end.

$$128 \times 10 = 1280$$

- We can do a similar thing in binary. Shifting left once multiplies by two.

$$11 \times 10 = 110 \quad (\text{in decimal, } 3 \times 2 = 6)$$

- Shifting left twice is equivalent to multiplying by four.

$$11 \times 100 = 1100 \quad (\text{in decimal, } 3 \times 4 = 12)$$

- Similarly, shifting once to the *right* is equivalent to *dividing* by two.

$$1100 / 10 = 100 \quad (\text{in decimal, } 12 / 2 = 6)$$

# Addition and multiplication summary

---

- Adder and multiplier circuits reflect human algorithms for addition and multiplication.
- Adders and multipliers are built **hierarchically**.
  - We start with **half adders** and **full adders** and work our way up.
  - Building these circuits from scratch using truth tables and K-maps would be pretty difficult.
- Adder circuits are limited in the number of bits that can be handled. An **overflow** occurs when a result exceeds this limit.
- There is a tradeoff between simple but slow **ripple carry adders** and more complex but faster **carry lookahead adders**.
- Multiplying and dividing by powers of two can be done with simple shifts.