 


# Arithmetic-logic units


---

- An **arithmetic-logic unit** or **ALU** performs many different arithmetic and logical operations. The ALU is at the “heart” of a processor—you could say that everything else in the computer is there to support the ALU.
- Today we’ll see how you can build your own ALU.
  - First we explain how several basic operations can be implemented using just an unsigned adder.
  - Then we’ll talk about logical operations and how to build a corresponding circuit.
  - Finally, we’ll put these two pieces together.
- We show the same examples as the book (pp. 360-365), but things are re-labelled to be clearer in LogicWorks. Some inputs (CI and S0) are also treated differently.


 
# It's the adder-subtractor again!


- An **arithmetic unit** is a circuit that supports several different arithmetic operations.
- We've already seen a simple arithmetic unit that supports two functions—addition and subtraction.
- That circuit has two four-bit data inputs **X** and **Y**, and a function selection input **Sub**.
- The four-bit output **G** is either  $X + Y$  or  $X - Y$ , depending on the value of the **Sub** input.



Sub	G
0	$X + Y$
1	$X - Y$
 
# Hierarchical circuit design


- This circuit is based on a four-bit unsigned adder, which *always* outputs the sum of its inputs,  $S = A + B + CI$ .
- To perform addition or subtraction, all we did was vary adder inputs  $A$ ,  $B$  and  $CI$  according to the arithmetic unit inputs  $X$ ,  $Y$  and  $Sub$ .
- The output  $G$  of the arithmetic unit comes right out of the adder.




Sub	Adder inputs			Adder output
	A	B	CI	S
0	Y	X	0	$X + Y$
1	$Y'$	X	1	$X - Y$
 
# Some more possible functions


- We can follow the same approach to implement other functions with our four-bit unsigned adder as well!



$S = X$  (transfer)

 

$S = X + 1$  (increment)

 

$S = X - 1$  (decrement)

A	B	CI	S
0	X	0	X (transfer)
0	X	1	X + 1 (increment)
-1	X	0	X - 1 (decrement)

# The role of CI

---

- Notice that for the transfer and increment operations, the adder has the same A and B inputs, and only the CI input differs.
- In general we can always create additional functions by setting CI = 0 instead of CI = 1, and vice versa.
- Another example involves subtraction.
  - We already know that two's complement subtraction is performed by setting  $A = Y'$ ,  $B = X$  and  $CI = 1$ , so the adder outputs  $X + Y' + 1$ .
  - If we keep  $A = Y'$  and  $B = X$ , but set CI to 0 instead, we get the output  $X + Y'$ . This turns out to be a *ones' complement* subtraction.



# Table of arithmetic functions

- Here are the different arithmetic operations we've seen so far, and how they can be implemented by an unsigned four-bit adder.
- There are actually just four basic operations, but by setting CI to both 0 and 1 we come up with eight operations.
- Notice that the transfer function can be implemented in two ways, and appears twice in this table.

Arithmetic operation $A + B + CI$		Required adder inputs		
		A	B	CI
X	(transfer)	0000	X	0
X + 1	(increment)	0000	X	1
X + Y	(add)	Y	X	0
X + Y + 1		Y	X	1
X + Y'	(1C subtraction)	Y'	X	0
X + Y' + 1	(2C subtraction)	Y'	X	1
X - 1	(decrement)	1111	X	0
X	(transfer)	1111	X	1

# Selection codes

- We can make a circuit that supports all eight of these functions, using just a single unsigned adder.
- First, we must assign a three-bit selection code  $S$  for each operation, so we can specify which function should be computed.

Selection code			Arithmetic operation $A + B + CI$	Required adder inputs		
$S_2$	$S_1$	$S_0$		A	B	CI
0	0	0	$X$ (transfer)	0000	X	0
0	0	1	$X + 1$ (increment)	0000	X	1
0	1	0	$X + Y$ (add)	Y	X	0
0	1	1	$X + Y + 1$	Y	X	1
1	0	0	$X + Y'$ (1C subtraction)	$Y'$	X	0
1	0	1	$X + Y' + 1$ (2C subtraction)	$Y'$	X	1
1	1	0	$X - 1$ (decrement)	1111	X	0
1	1	1	$X$ (transfer)	1111	X	1

# Generating adder inputs


- The circuit for our arithmetic unit just has to generate the correct inputs to the adder (**A**, **B** and **CI**), based on the values of **X**, **Y** and **S**.
  - Adder input **CI** should always be the same as selection code bit **S0**.
  - The adder's input **B** is always equal to **X**.
  - Adder input **A** depends only on **S2**, **S1** and **Y**.

Selection code			Arithmetic operation		Required adder inputs		
S2	S1	S0	A + B + CI		A	B	CI
0	0	0	X	(transfer)	0000	X	0
0	0	1	X + 1	(increment)	0000	X	1
0	1	0	X + Y	(add)	Y	X	0
0	1	1	X + Y + 1		Y	X	1
1	0	0	X + Y'	(1C subtraction)	Y'	X	0
1	0	1	X + Y' + 1	(2C subtraction)	Y'	X	1
1	1	0	X - 1	(decrement)	1111	X	0
1	1	1	X	(transfer)	1111	X	1


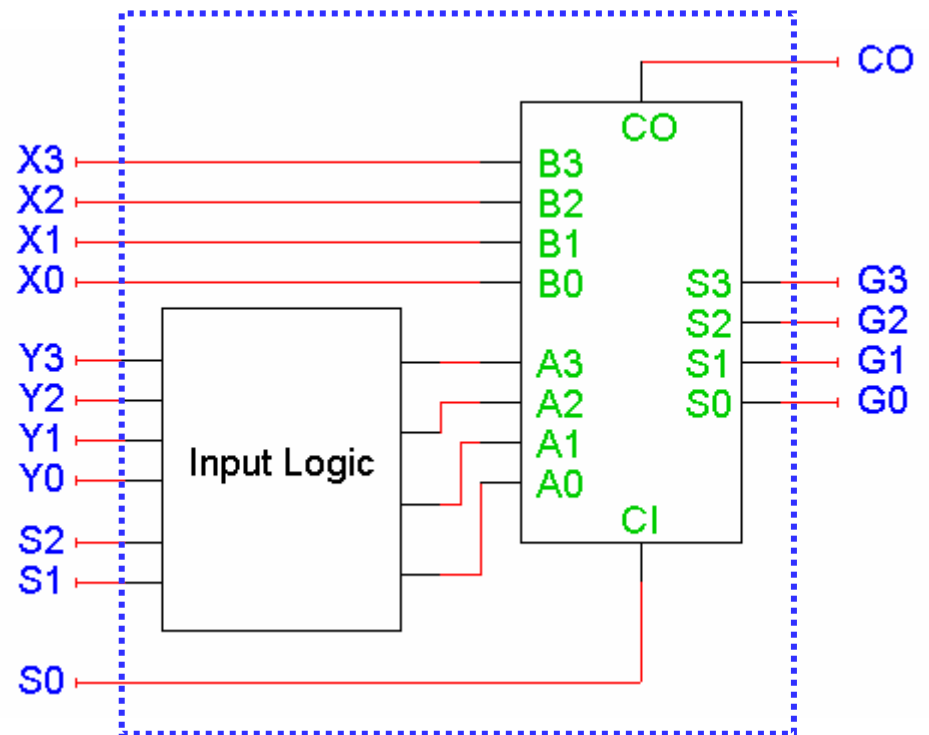
# Building the input logic

- Here is a diagram of our arithmetic unit so far.
- We've already set the adder inputs **B** to **X** and **CI** to **S0**, as explained on the previous page.
- All that's left is to generate adder input **A** from the arithmetic unit input **Y** and the function selection code bits **S2** and **S1**.
- From the table on the last page, we can see that adder input **A** should be set to 0000, **Y**, **Y'** or 1111, depending on **S2** and **S1**.




S2	S1	A
0	0	0000
0	1	Y
1	0	Y'
1	1	1111

# Primitive gate-based input logic

- We'll build this circuit using primitive gates.
- If we want to use Karnaugh maps for simplification, then we should first expand the abbreviated truth table, since the  $Y$  in the output column is actually an input.
- Remember that  $A$  and  $Y$  are each four bits long! We are really describing *four* functions,  $A_3$ ,  $A_2$ ,  $A_1$  and  $A_0$ , but they are each generated from  $Y_3$ ,  $Y_2$ ,  $Y_1$  and  $Y_0$  in the same way.

S2	S1	A
0	0	0000
0	1	Y
1	0	Y'
1	1	1111

 

S2	S1	$Y_i$	$A_i$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


# Primitive gate implementation

- We can find a minimal sum of products from the truth table.


		S1		
	0	0	1	0
S2	1	0	1	1
		Y <sub>i</sub>		

$$A_i = S2 Y_i' + S1 Y_i$$

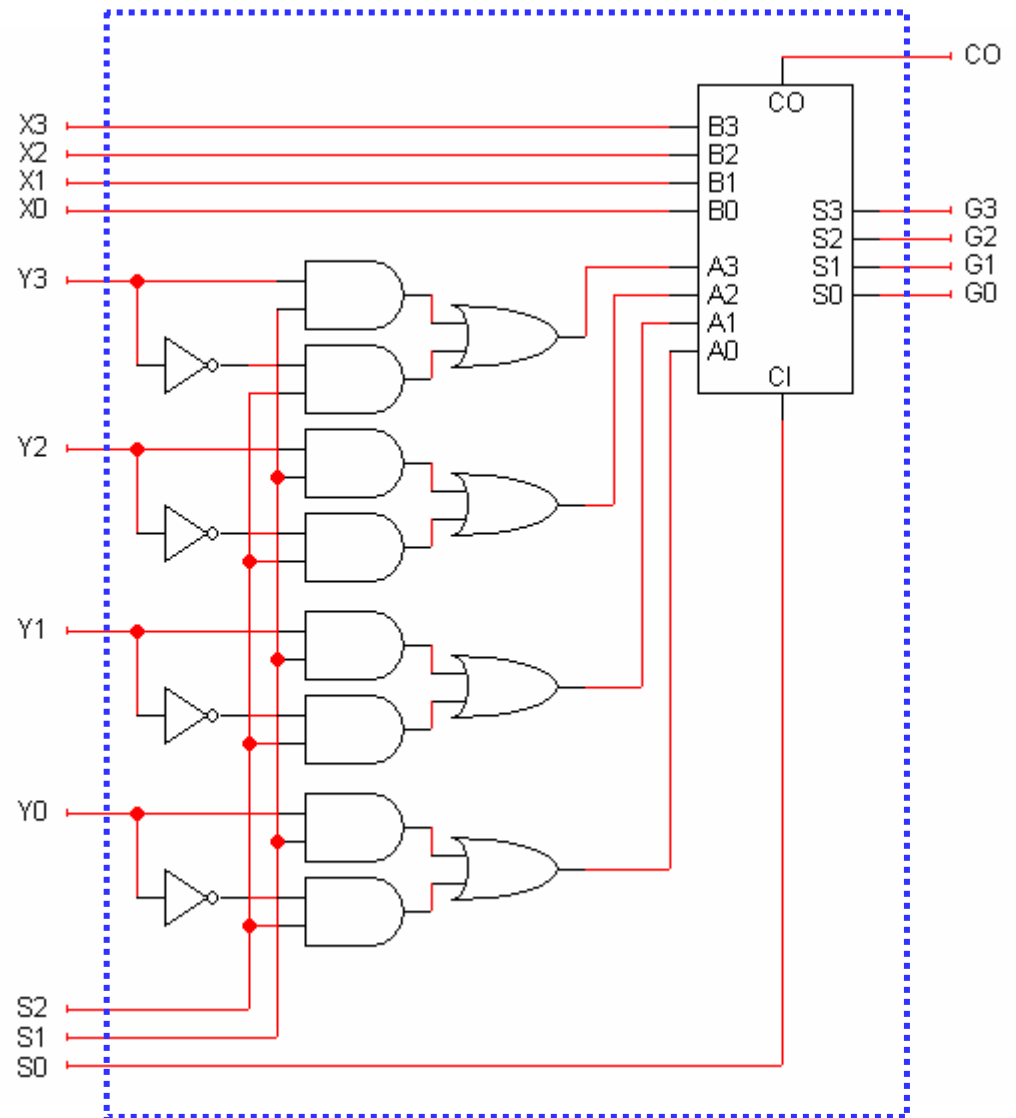
- Again, we have to repeat this once for each adder input bit A3-A0.
- You can see this repetition in the circuit diagram here.



# Our complete arithmetic unit

 

S2	S1	S0	G
0	0	0	X
0	0	1	X + 1
0	1	0	X + Y
0	1	1	X + Y + 1
1	0	0	X + Y'
1	0	1	X + Y' + 1
1	1	0	X - 1
1	1	1	X

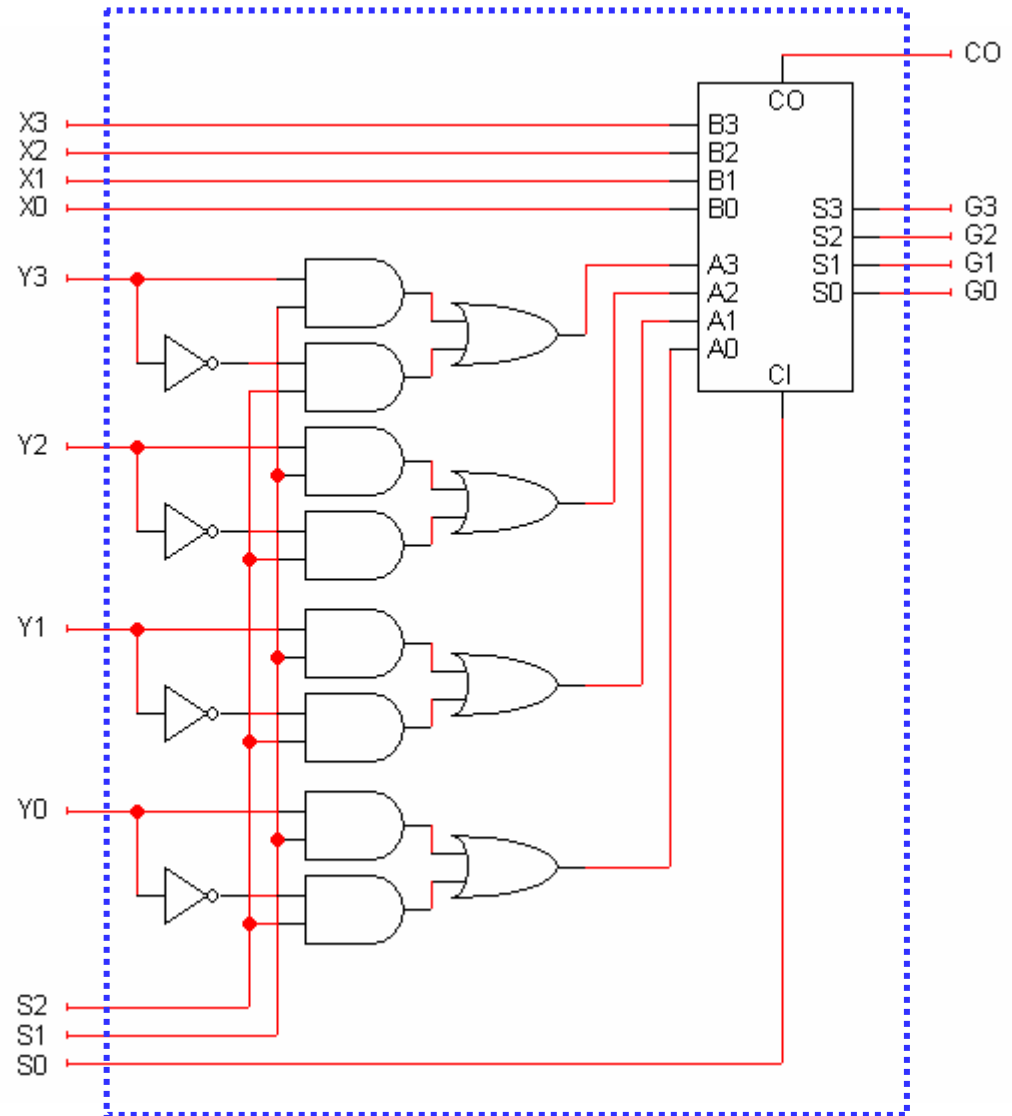

# Bitwise logical operations

---

- Most computers also support logical operations like AND, OR and NOT, but extended to multi-bit **words** instead of just single bits.
- To apply a logical operation to two words X and Y, apply the operation on each pair of bits  $X_i$  and  $Y_i$ .

$$\begin{array}{r} \phantom{\text{AND}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \phantom{\text{AND}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \text{AND} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \phantom{\text{AND}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \phantom{\text{AND}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \end{array}$$

$$\begin{array}{r} \phantom{\text{OR}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \phantom{\text{OR}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \text{OR} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \phantom{\text{OR}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \phantom{\text{OR}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \end{array}$$

$$\begin{array}{r} \phantom{\text{XOR}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \phantom{\text{XOR}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \text{XOR} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \phantom{\text{XOR}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \\ \phantom{\text{XOR}} \phantom{\underline{\phantom{1} \phantom{0} \phantom{1} \phantom{1}}} \end{array}$$

- We've already seen this informally in two's complement arithmetic, when we talked about complementing all the bits in a number.

# Bitwise operations in programming

---

- Languages like C, C++ and Java provide bitwise logical operations.

$\&$  (AND)             $|$  (OR)             $\wedge$  (XOR)             $\sim$  (NOT)

- These operations treat each integer as a bunch of individual bits.

$13 \& 25 = 9$             (because  $01101 \& 11001 = 01001$ )

- They are *not* the same as the C operators  $\&\&$ ,  $||$  and  $!$ , which treat each integer as a single logical value (0 is false, everything else is true).

$13 \&\& 25 = 1$             (because  $\text{true} \&\& \text{true} = \text{true}$ )

- Bitwise operators are often used in programs to set a bunch of Boolean options, or flags, with one argument. For instance, to initialize a double-buffered, RGB-mode window with a depth buffer using OpenGL:

```
glutInitDisplayMode(GLUT_DOUBLE | GLUT_RGBA | GLUT_DEPTH);
```

# Bitwise operations in networking

---

- IP addresses are actually 32-bit binary numbers, and bitwise operations can be used to find network information.
- For example, you can bitwise-AND an address like 192.168.10.43 with a “subnet mask” to find the “network address,” or which network the host is connected to.

$$\begin{array}{r} 192.168.10.43 = 11000000.10101000.00001010.00101011 \\ \& \underline{255.255.255.224 = 11111111.11111111.11111111.11100000} \\ 192.168.10.32 = 11000000.10101000.00001010.00100000 \end{array}$$

- You can use bitwise-OR to generate a “broadcast address” for sending data to all machines on a local network.

$$\begin{array}{r} 192.168.10.43 = 11000000.10101000.00001010.00101011 \\ | \quad 0.0.0.31 = 00000000.00000000.00000000.00011111 \\ \hline 192.168.10.63 = 11000000.10101000.00001010.00111111 \end{array}$$

# Defining a logic unit

---

- A **logic unit** implements different logical functions on two multi-bit inputs  $X$  and  $Y$ , producing an output  $G$ .
- We'll design a simple four-bit logic unit that supports four operations.

S1	S0	G
0	0	$XY$
0	1	$X + Y$
1	0	$X \oplus Y$
1	1	$X'$

- Again, we have to assign a selection code  $S$  for each possible function.




# Implementing bitwise operations


- Bitwise operations are applied to pairs of corresponding bits from inputs  $X$  and  $Y$ , so we can generate each bit of the output  $G$  in the same way.

S1	S0	$G_i$
0	0	$X_i Y_i$
0	1	$X_i + Y_i$
1	0	$X_i \oplus Y_i$
1	1	$X_i'$




 
- We can implement each output bit  $G_i$  as shown on the right, using a multiplexer to select the desired primitive operation.
- The complete logic unit diagram is given on the next page.



# Our complete logic unit

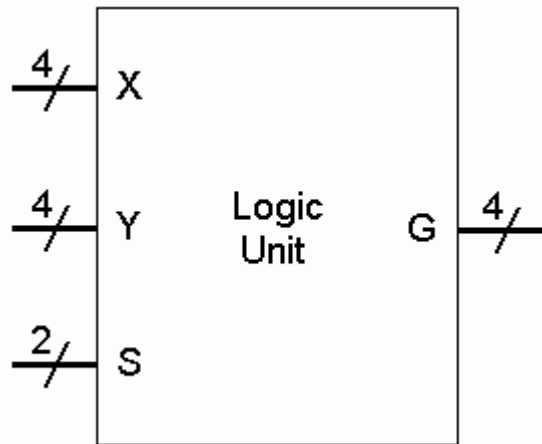

S1	S0	G
0	0	$XY$
0	1	$X + Y$
1	0	$X \oplus Y$
1	1	$X'$

    


# Combining the arithmetic and logic units

- We can combine our arithmetic and logic units into a single **arithmetic-logic unit**, or **ALU**.
  - The ALU will accept two data inputs **X** and **Y**, and a selection code **S**.
  - It outputs a result **G**, as well as a carry out **CO** (only useful for the arithmetic operations).
- Since there are twelve total arithmetic and logical functions to choose from, we need a four-bit selection input.
- We've added selection bit **S3**, which chooses between arithmetic (**S3=0**) and logical (**S3=1**) operations.

S3	S2	S1	S0	G
0	0	0	0	X
0	0	0	1	X + 1
0	0	1	0	X + Y
0	0	1	1	X + Y + 1
0	1	0	0	X + Y'
0	1	0	1	X + Y' + 1
0	1	1	0	X - 1
0	1	1	1	X
1	x	0	0	X and Y
1	x	0	1	X or Y
1	x	1	0	X xor Y
1	x	1	1	X'

# A complete ALU circuit

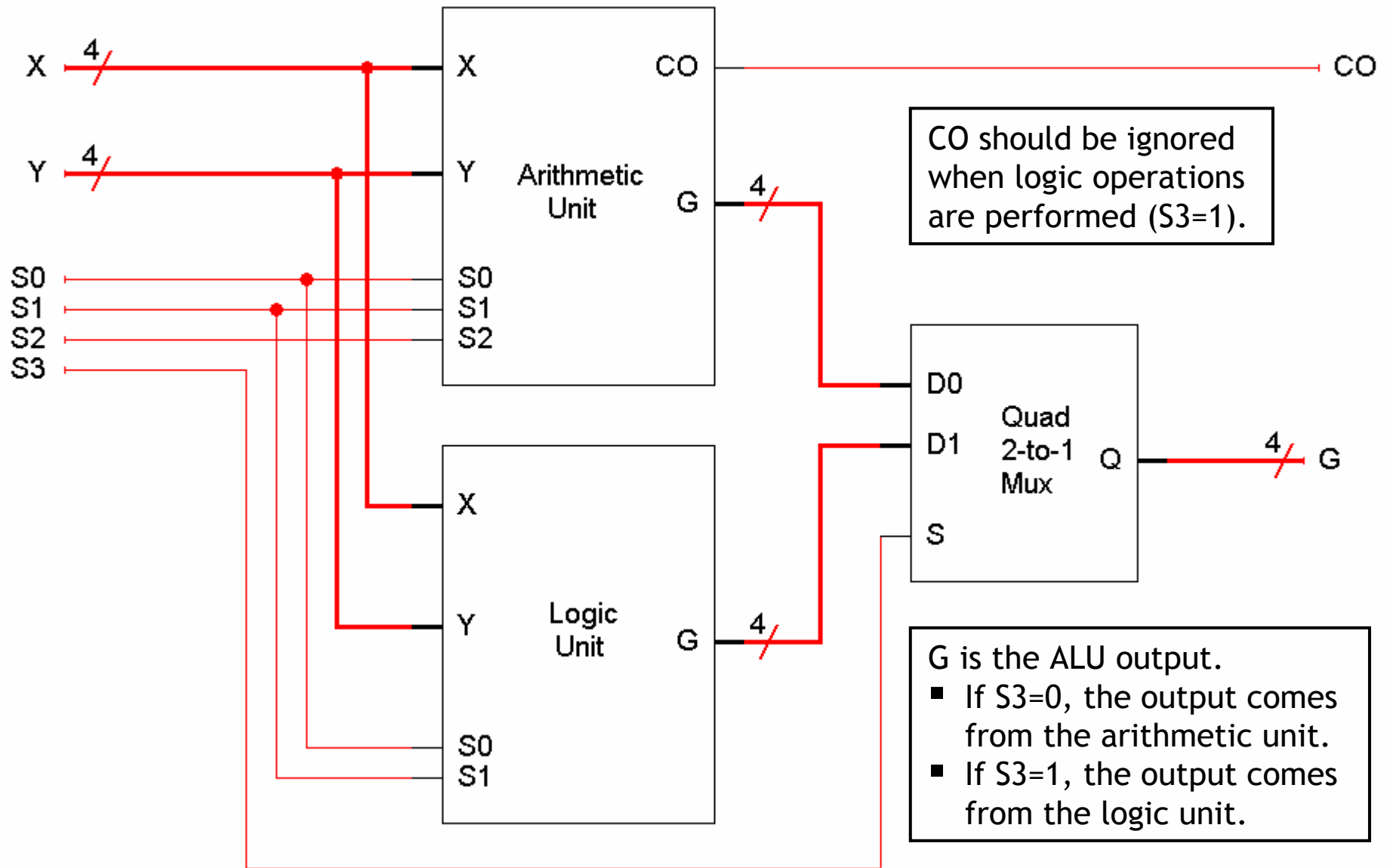


# Comments on the multiplexer

---

- Both arithmetic and logic units are “active” and produce outputs.
  - The multiplexer determines whether the final result  $G$  comes from the arithmetic or logic unit.
  - The output of the other one is ignored.
- In programming, you’d use an if-then statement to select one operation or the other. This is useful since programs execute serially, and we want to avoid unnecessary work.
- Our hardware scheme may seem like wasted effort, but it’s not really.
  - Disabling one unit or the other wouldn’t save that much time.
  - We have to build the hardware for both units anyway.
  - You can think of this as a form of parallel processing, where several operations are done together.
- This is a very common use of multiplexers in logic design.

# An external view of the ALU

 

S3	S2	S1	S0	G
0	0	0	0	X
0	0	0	1	X + 1
0	0	1	0	X + Y
0	0	1	1	X + Y + 1
0	1	0	0	X + Y'
0	1	0	1	X + Y' + 1
0	1	1	0	X - 1
0	1	1	1	X
1	x	0	0	X and Y
1	x	0	1	X or Y
1	x	1	0	X xor Y
1	x	1	1	X'

# Summary

---

- In the last few lectures we looked at various arithmetic issues.
  - You can build adders hierarchically, starting with half adders.
  - A good representation of negative numbers simplifies subtraction.
  - Unsigned adders can implement many other arithmetic functions.
  - Logical operations can be applied to multi-bit values.
- Where are we now?
  - We started at the very bottom with primitive gates, but now we can understand ALUs, a critical part of any processor.
  - This all built upon our knowledge of Boolean algebra, Karnaugh maps, multiplexers, circuit analysis and design, and data representations.

