

Datapaths




- The rest of the semester focuses on **computer architecture**—combining combinational and sequential circuit elements to produce a computer.
- We'll spend most of our time on the **central processor unit** or **CPU**.
 - The **datapath** does all of the actual data processing.
 - A **control unit** tells the datapath what to do and when to do it.
 - An **instruction set** is the programmer's interface to the CPU.
- Today will be devoted to the datapath.

Keep it simple!

- *Abstraction* is very helpful in understanding processors.
 - Although we studied how devices like registers and muxes are built, we don't need that level of detail here.
 - You should focus more on *what* these component devices are doing, and less on *how* they work.
- Otherwise it's easy to get bogged down in the details, and datapath and control units can be a little intimidating.




A basic CPU model

 

- A processor is just one big sequential circuit.
 - Some registers are used to store values, which form the state.
 - An ALU performs various operations on the stored data.
- CS375 and other theory courses talk more about state machines and how they can model computers.

Register transfers

 

- The processor just moves data between registers, possibly with some ALU computations.
- To describe this data movement and computation more precisely, we'll introduce a **register transfer language**.
 - The objects in the language are *registers*.
 - The basic operations are *transfers*, in which data is copied from one register to another.
 - We can also perform arithmetic operations on data being transferred.

Register transfer language

- Two-character names denote **registers**, such as R0, R1, DR, or SA.
- Arrows indicate **data transfers**. For example, we can copy the contents of **source register** R2 into the **destination register** R1 in one clock cycle.

R1 ← R2

- A **conditional transfer** is performed only if the Boolean condition in front of the operation is true. Below, we transfer R3 to R2 only when K = 1.

K: R2 ← R3

- **Multiple transfers** on the *same* clock cycle are separated by commas.

R1 ← R2, K: R2 ← R3

Register transfer operations

- We can apply **arithmetic operations** to registers.

$$\begin{aligned} R1 &\leftarrow R2 + R3 \\ R3 &\leftarrow R1 - 1 \end{aligned}$$


- **Bitwise logical operations** can be expressed. We use special symbols for AND and OR to prevent confusion with arithmetic operations.

$$\begin{aligned} R2 &\leftarrow R1 \wedge R2 && \text{bitwise AND} \\ R3 &\leftarrow R0 \vee R1 && \text{bitwise OR} \end{aligned}$$

- Finally, we can **shift** values left or right by one bit. The source register is not modified, and we assume that the shift input is always 0.

$$\begin{aligned} R2 &\leftarrow sl R1 && \text{left shift} \\ R2 &\leftarrow sr R1 && \text{right shift} \end{aligned}$$


What's inside the datapath?

 

- Now we'll look in detail at the processor's **datapath**, which is responsible for doing all of the dirty work.
 - An ALU does computations, as we've seen before.
 - A limited set of registers serves as fast temporary storage.
 - A larger, but slower, random-access memory is also available.

The all-important ALU

- The main job of a central processing unit is to “process,” or to perform computations... Remember the ALU from a few weeks ago?
- We’ll use the following general block symbol for the ALU.
 - **A** and **B** are two n -bit numeric inputs.
 - **FS** is an m -bit function select code, which picks one of 2^m functions.
 - The n -bit result is called **F**.
 - Several **status bits** provide more information about the output **F**.
 - **V = 1** for signed overflow.
 - **C** is the carry out.
 - **N = 1** if the result is negative.
 - **Z = 1** if the result is 0.
- This should all look familiar from MP2!

 


ALU functions

- For concrete examples, we'll use the ALU as it's presented in the textbook.
- The table of operations on the right is taken from page 373.
- The function select code FS is 5 bits long, but there are only 15 different functions here.
- We use different symbols for AND and OR to avoid confusion with arithmetic operations.

FS	Operation
00000	$F = A$
00001	$F = A + 1$
00010	$F = A + B$
00011	$F = A + B + 1$
00100	$F = A + B'$
00101	$F = A + B' + 1$
00110	$F = A - 1$
00111	$F = A$
01000	$F = A \wedge B$ (AND)
01010	$F = A \vee B$ (OR)
01100	$F = A \oplus B$
01110	$F = A'$
10000	$F = B$
10100	$F = sr B$ (shift right)
11000	$F = sl B$ (shift left)


Register files

 - As we mentioned already, the ALU inputs and outputs will come from and go to a set of registers.
- Here is a block symbol for a $2^k \times n$ register file.
 - There are 2^k registers, so each register address is k bits long.
 - Each register contains an n -bit value, so the data inputs and outputs have to be n bits wide.




Accessing the register file

- You can read *two* registers at once by supplying the **AA** and **BA** inputs. The data appears on the **A** and **B** outputs.
- You can write to a register by using the **DA** and **D** inputs, and setting **WR = 1**.
- These are registers so there must be a clock signal, even though we usually don't show it in diagrams.
 - You can read from the register file at any time.
 - Data is written only on the positive edge of the clock.

 


What's inside the register file

 - Here's a $4 \times n$ register file. (We'll assume a $4 \times n$ register file for all our examples today.)




Explaining the register file

 

- This block diagram represents an n -bit register.
 - When **Load = 1**, the data input is stored into the register.
 - When **Load = 0**, the register just keeps its current value.
- The 2-to-4 decoder selects one of the four registers for writing. If **WR = 1**, the decoder will be enabled and one of the Load signals will be active.
- The n -bit 4-to-1 muxes select the two register file outputs A and B, based on the inputs AA and BA.

My first datapath

- So here is the most basic datapath.
 - The ALU's two data inputs come from the register file.
 - The ALU computes a result, which is saved back to the registers.
- **WR**, **DA**, **AA**, **BA** and **FS** are **control signals**. Their values determine the exact actions taken by the datapath— which registers are used and for what operation.
- Remember that many of the signals here are actually multi-bit values!

 


An example computation

- Let's look at the proper control signals for the operation below.


$$R0 \leftarrow R1 + R3$$

 - Set $AA = 01$ and $BA = 11$. This causes the value in R1 to appear at **A data**, and the value in R3 to appear at the output **B data**.
- Set the ALU function select input $FS = 00010$, to perform the addition $A + B$.
- Set $DA = 00$ and $WR = 1$. On the next positive clock edge, the ALU's result ($R1 + R3$) will be stored in R0.




Two questions

 - Four registers isn't a lot. What if we need more storage?
- Who exactly decides which registers are read and written and which ALU function is executed?




Reading from RAM

- To *read* from RAM, **A data** must supply an address, and we also need to ensure $MW = 0$.
- The RAM output should be sent to the register file for storage.
- This means that the register file's **D data** input could come from *either* the ALU output or the RAM.
- A new multiplexer **MD** selects a source for the register file.
 - If $MD = 0$, the ALU output can be stored in the register file.
 - If $MD = 1$, the RAM output is sent to the registers instead.

 


Notes about this setup

- We now have a way to copy data between our register file and the RAM.
- Notice that there's no way for the ALU to directly access the memory—RAM values *must* go through the register file first.
- Here the size of the memory is limited by the size of the registers; with n -bit registers, we can only use a $2^n \times n$ RAM.
- For simplicity we'll assume the RAM is at least as fast as the CPU clock, even though this is not exactly true in real life.

 

Memory transfer notation

 - In our transfer language, the contents of random access memory address X are denoted as $M[X]$. Here are two examples.
 - The first word in RAM is $M[0]$.
 - If register $R1$ holds an address, then $M[R1]$ is the data at that address.
- The $M[]$ notation is like a pointer dereference operation in C or C++.



Example sequence of operations


- Here is a simple series of register transfer instructions.

```
R3 ← M[R0]
R3 ← R3 + 1
M[R0] ← R3
```

- This just increments the value stored at address R0 in RAM.
 - R0 is the first register in our register file. We'll assume it contains a valid memory address.
 - Again, our ALU only operates on registers, so the RAM contents must first be loaded into a register, and then saved back to RAM.
- We can perform these three register transfer operations in our datapath over three consecutive clock cycles.


R3 ← R3 + 1

 - **AA = 11**, so R3 is read from the register file and directed to the ALU's A input.
- **FS** needs to be 00001 for the operation A + 1. Then, R3 + 1 appears as the ALU output F.
- If **MD** is set to 0, this output will go back to the register file.
- To write to R3, we need to set **DA = 11** and **WR = 1**.
- Again, **MW** should be 0 so that RAM contents aren't changed.
- We didn't use BA.




$M[R0] \leftarrow R3$

 - Finally, we must store the value of R3 into RAM address R0.
- The memory address comes from “A data” and the contents come from “B data.” We have to set $AA = 00$ and $BA = 11$, to send R0 to ADRS and R3 to DATA.
- MW must be 1 to write to RAM.
- No register updates are needed, so WR should be 0, which means MD and DA are unused.
- We also didn’t need the ALU, so FS can be ignored.




Constant in

 - One last addition to our basic datapath is a **Constant** input.
- The revised datapath is shown here, with a new multiplexer and control signal **MB**.
- We'll see how this is used later. Intuitively, it provides an easy way to initialize a register or memory location with an arbitrary number.



Control units

- From these examples, you can see that different actions can be performed by providing different inputs for the datapath control signals.
- The two multiplexers MB and MD help us select from one of several sources, just like the muxes in the register transfer lecture last time.
- The second question we had was “Who exactly decides which registers are read and written, and which ALU function is executed?”
 - In real computers, datapath actions are determined by the **program** that’s loaded and running.
 - A **control unit** is responsible for generating the correct control signals for a datapath, based on the program code.
- We’ll talk about programs next week, and then control units the week after that.

 

Summary

- A processor's basic job is to move data between registers, possibly with some ALU computations.
- We presented a **register transfer language** for describing computation and movement of data between registers.
- The **datapath** is the part of a processor where this is all done.
 - The basic components are an ALU, a register file and some RAM.
 - The ALU does all of the computations, while the register file and RAM provide storage for the ALU's operands and results.
- Various **control signals** in the datapath determine its behavior.
- Next we'll see how programmers give commands to the processor, and how those commands are translated in control signals for the datapath.

